

HDLRuby Tutorial for Software People

In this tutorial, you will learn the basics about the description of digital circuits using HDLRuby from the software point of view. In detail you will learn:

1. [What is HDLRuby and how to use its framework.](#)
2. [How to represent a circuit.](#)
3. [How to describe an algorithm to be implemented by a circuit.](#)
4. [How to add parallelism to your algorithms.](#)
5. [Toward lower level hardware design: the processes.](#)
6. [Not enough? What about genericity, object orientation, metaprogramming, and reflection?](#)

Within these topics, you will also have an explanation of how the following high-level concepts can be used in HDLRuby:

- Object-oriented programming
- Reflection
- Genericity
- Metaprogramming

But, before going further, here are a few...

Prerequisites

Since this tutorial is aimed at software people, it is assumed you have a good understanding of programming and the relevant tools (e.g., editor, compiler). However, it is not assumed that you have any knowledge about digital hardware design. Otherwise, knowing the Ruby programming language is recommended but not mandatory.

To use HDLRuby the following software is required:

- A distribution of the Ruby language.
- A text editor. If you like syntax highlighting or other fancy features, please choose one supporting Ruby.
- A command line interface (e.g., command prompt, terminal emulator).

The following software is also recommended:

- A wave viewer supporting *vcd* files (e.g., [GTKWave](#))

1. What is HDLRuby and how to use its framework


HDLRuby is a hardware description language (HDL) based on the Ruby programming language. It is implemented as a Ruby library so that, by construction, any Ruby code can be used and executed within the HDLRuby description.

Before going further, let us briefly explain what is a [HDL](#). Then, more details will be given about how to [install HDLRuby](#) and how to [use it](#).

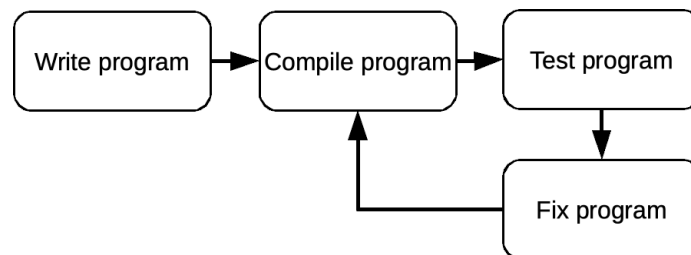
1.1. What is a hardware description language (HDL)

A hardware description language (HDL) is a formal language similar to programming languages that are used for describing electronic circuits. Such circuits can be divided into two categories: analog circuits and digital circuits. While there exists HDL for describing the first category of circuits, a large majority of them only support the second one so in practice, HDL means actual language for describing digital circuits only. Among the multiple HDL, two became de-facto standards: Verilog HDL and VHDL.

HDL are there to helping producing circuits. Nowadays, there exist powerful software tools that can automatically produce circuits from HDL descriptions. However, like in software, there may be errors in the descriptions, or they may be sub-optimal, so that the final circuit does not work, or does not meet some constraints. Unfortunately, in hardware, producing a circuit is very time-consuming and expensive so contrary to software, errors or low-performance results must be avoided as early as possible. This is why it is common in hardware to **simulate** your circuit description before starting to produce it. In other words, while in software it is common to perform the following loop:



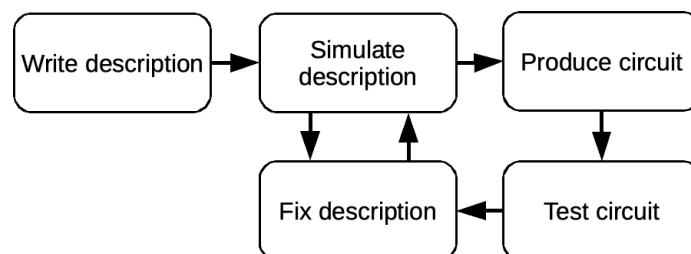In hardware, the design loop is more like as follows:



At first, the HDL have the same look and feel compared to classical programming languages like C or Java: they include expressions, control statements, and kind of variables. However, the underlining model of computation is quite different, especially because circuits are inherently parallel devices, but this will be explained progressively during this tutorial. For now, it is enough to remember the following:

- HDL are used for describing digital circuits and the most common ones are Verilog HDL and VHDL.
- Using software tools called synthesis tools, you can produce real digital circuits from HDL description. But before that, you will need to simulate your description.
- HDL looks like a common programming language but does not work the same.

And what about HDLRuby?

Well, HDLRuby is an HDL for describing digital circuits like Verilog HDL or VHDL but aiming at being more flexible and productive than them by relying on many concepts inherited from the Ruby programming language. So everything said earlier about HDL applies to HDLRuby, but we try to make it much easier for the designers.

1.2. Installing HDLRuby

HDLRuby is distributed as a RubyGems package. It can therefore be installed using the following command:

```
gem install HDLRuby
```

If everything is OK the following should be displayed:

```
Fetching HDLRuby-<version>.gem
Building native extensions. This could take a while...
Successfully installed HDLRuby-<version>
Parsing documentation for HDLRuby-<version>
Done installing documentation for HDLRuby after <x> seconds.
```

The `version` number should be the latest version of HDLRuby.

You can then check if HDLRuby is properly installed by using the following command:

```
hdrcc --version
```

And the result should be:

```
<version>
```

If the resulting `version` number does not match the install number, there may have been a problem somewhere. It may be a good idea to close the terminal or command prompt and try again the command in a new one.

1.3. Using HDLRuby

Up to now, we said that HDLRuby is a language, it is in truth a complete framework for designing and simulating digital circuits. It includes several compilers, simulators, and libraries that are all accessible through a single command: `hdrcc`.

Basically, `hdrcc` is used as follows:

```
hdrcc <options> <input file> <output directory>
```

Where `options` specifies the action to be performed, `input file` specifies the input HDLRuby file, and `output directory` specifies the directory where the command results will be saved. As a general rule, when an input file is specified, an output directory must also be specified.

Several actions are possible using `hdrcc`, the main ones being the followings:

- Simulate a circuit description:

```
hdrcc --sim <input file> <output directory>
```

- Generate the equivalent Verilog HDL code:

```
hdrcc --verilog <input file> <output directory>
```

This second action is necessary if you want to produce a real circuit since HDLRuby is not yet supported by synthesis tools.

Note: VHDL generation is also possible using the following command:

```
hdrcc --vhdl <input file> <output directory>
```

However, the Verilog HDL output is tested more often than the VHDL one (for practical reasons) and is therefore more reliable.

And that's it! For details about all the actions that can be performed, how to write an input file, and what kind of output can be produced, let us see the remaining of the tutorial.


2. How to represent a circuit in HDLRuby

In this section we will see:

- [How to declare a circuit.](#)
- [How to reuse a circuit already declared.](#)

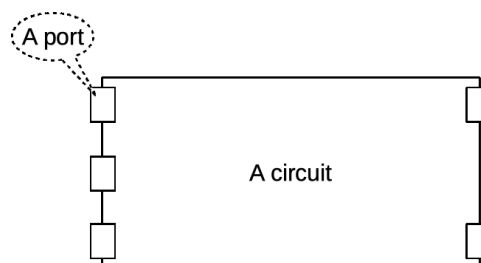2.1. Declaring a circuit

In HDLRuby as well as in other HDL, a circuit is viewed as a box that communicates with its environment with ports. The following charts illustrate such a view with a circuit including 6 ports:



However, ports are not simple entry points since they have a data type and a direction that can be one of the following:

- `input` : such a port can only be used for transmitting data from the outside of the circuit to its inside.
- `output` : such a port can only be used for transmitting data from the inside of the circuit to its outside.
- `inout` : such a port can only be used both as an `input` port and as an `output` port. Due to physical limitations, these ports are difficult to use though, and will therefore be ignored until the [advance part of this tutorial](#).

That's all very well, but when do I write HDLRuby code?


With that in mind, declaring a circuit consists in specifying its name and its ports. In HDLRuby this is done as follows:

```
system :my_circuit do
  input :clk, :rst
  [16].input :addr
  input :ce
  [8].input :data_in
  [8].output :data_out
end
```

So please write the code above in a file called (for example) `my_circuit.rb` , and let us explain its meaning.

- In the first line, the keyword `system` indicates a new circuit will be described. Its name is given after the colon, `my_circuit` here.
- The `do` → `end` block contains the description of the circuit. Here, only the ports are specified as follows:
 - On the second line, `input` specifies two one-bit input ports named respectively `clk` and `rst` .
 - The third line specifies a 16-bit input port named `addr` .
 - The fourth line specifies a one-bit input port named `ce` .
 - The fifth line specifies an eight-bit input port named `data_in` .
 - The sixth line specifies an 8-bit output port named `data_out` .

And here is a diagram of this circuit:

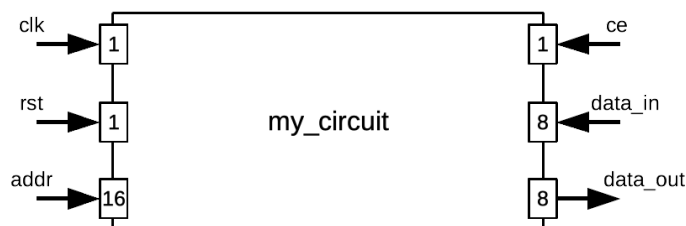

To sum up things:

- `system` declares a new circuit description.
- `input` specifies one or several input ports, `output` one or several output ports, and `inout` one or several input-output ports.
- The data type of the port is given before the direction as follows:

`<type>.input <list of ports names>`

We will give later more details about data types in HDLRuby.

Now let us see if your circuit description is all right with the following command:

```
hdrcc my_circuit.rb work
```

...Nothing happened? Great, that means that there was no syntax error in your description. Now let us try something else:

```
hdrcc --hdr my_circuit.rb work
```

If everything was OK, a file named `my_circuit.rb` should have appeared in the `work` directory. Open it with a text editor, its content should be the following:

```

system : "__:T:0:1" do
  bit. input :clk
  bit.input :rst
  bit[15..0].input :addr
  bit.input :ce
  bit[7..0].input :data_in
  bit[7..0].output :data_out

end

```

It looks somewhat similar to the code you have just written. This is because it is the internal representation (IR) of your circuit in HDLRuby. You can see that the name of the circuit changed to some weird character string and that the data types also changed. The name is for avoiding name clashes, so you do not need to be concerned about it. The data types are low-level representations of the same data types that were used in the initial file. Still, this low-level representation is very close to the original one, but that will be less and less the case as the features are added to the circuit.

Now, out of curiosity, how will look the equivalent Verilog HDL code? For checking that just type the following command:

```
hdrcc --verilog my_circuit.rb work
```

If everything was OK, a file named `my_circuit.v` should have appeared in the `work` directory. Open it with a text editor, its content should be the following:

```

`timescale 1ps/1ps

module _v0_1( _v1_clk, _v2_rst, _v3_addr, _v4_data_in, _v5_data_out );
  input _v1_clk;
  input _v2_rst;
  input [15:0] _v3_addr;
  input _v4_ce;
  input [7:0] _v5_data_in;
  output [7:0] _v6_data_out;

endmodule

```

The syntax looks indeed a little bit different from HDLRuby, but you should be able to recognize the description of the circuit. The name of the ports is different though, this is because HDLRuby supports any UNICODE character for names and to avoid compatibility problems, recreates the names when generating Verilog. Still, an effort is made to keep the original name, e.g., `clk` became `_v1_clk`. But, just for the fun, please replace `:addr` in the HDLRuby file with `:@` and regenerate Verilog HDL from it... It works! And the result is:

```

`timescale 1ps/1ps

module _v0_1( _v1_clk, _v2_rst, _v3_, _v4_data_in, _v5_data_out );
  input _v1_clk;
  input _v2_rst;
  input [15:0] _v3_;
  input _v4_ce;
  input [7:0] _v5_data_in;
  output [7:0] _v6_data_out;

endmodule

```

Unfortunately, there is no more smiling face. This is because Verilog HDL only supports a subset of ASCII for names. But even without smiling, the code is valid because the HDLRuby framework did recreate Verilog HDL-friendly names.

2.2. How to reuse a circuit already declared

Like with functions in software, a circuit is often used as part of one or several larger circuits. Contrary to the software, however, the circuit must be physically copied for being reused. This copy is called an *instance* and the act of copying an *instantiation*. In HDLRuby, an instantiation is done as follows:

```
<circuit name>(:<copy name>)
```

For example, if you want to use copies of the previously defined circuit `my_circuit` in a new circuit called `another_circuit` you can do as follows:

```

system :another_circuit do
  input :clk, :rst
  [16].input :addr
  input :ce0, :ce1
  [8].input :data_in
  [8].output :data_out

  my_circuit(:my_circuit0)
  my_circuit(:my_circuit1)
end

```

For testing purposes, write the code above into another file called `another_circuit.rb`, and try to generate Verilog HDL from it:

```
hdrcc --verilog another_circuit.rb work
```

Oh, it appears that something went wrong since the following should have appeared:

```
another_circuit.rb:8:in `block in <main>': undefined HDLRuby construct, local variable or method `my_circuit'.
```

This error message indicates that `my_circuit` is not known. This is because, like the Ruby language, in HDLRuby you must specify the files you are using. Please add as the first line in your `another_circuit.rb` file the following code:

```
require_relative "my_circuit.rb"
```

Then retry the Verilog HDL generation command:

```
hdrcc --verilog another_circuit.rb work
```

Three new files should have appeared in the `work` directory: `_v10_5.v`, `_v8_4.v` and `another_circuit.v`. If you open the third file you should see:

```
`timescale 1ps/1ps

module _v0_3( _v1_clk, _v2_rst, _v3_addr, _v4_ce0, _v5_ce1, _v6_data_in,
_v7_data_out );
    input _v1_clk;
    input _v2_rst;
    input [15:0] _v3_addr;
    input _v4_ce0;
    input _v5_ce1;
    input [7:0] _v6_data_in;
    output [7:0] _v7_data_out;

    _v8_4 _v9_my_circuit0();
    _v10_5 _v11_my_circuit1();

endmodule
```

Again, we can see similarities between the resulting Verilog HDL code and the original HDLRuby one. Still, what are `_v8_4` and `_v10_5`? You can see them by opening the corresponding files `_v8_4.rb` and `_v10_5.rb`, those are the descriptions of `my_circuit` in Verilog HDL.

But why two of them? I would like to answer that this is because of a limitation of Verilog HDL, but this is not the case. It is because HDLRuby's instantiation mechanism is very different from the Verilog HDL (and the VHDL) one, so for the moment, and only for easing the coding work of the HDLRuby compiler, one description of `my_circuit` is generated per instance.

Copying a circuit is easy, but it achieves no purpose if the copied circuit is not in a relationship with its environment. It is where the ports become useful: they are the communication points between a circuit and its outside world. Concretely, to interact with a circuit, its ports must be connected to something that will interact with them. How this interaction work is a story for other sections, e.g., the one about [algorithms](#), about the [environnement](#), and the one about [behaviors](#). For now, let us focus on connection: in HDLRuby this is done using the assignment operator `<=` as follows:

- For an input port of the current circuit:

```
<something> <= <input port>
```

- For an output port of the current circuit:


```
<output port> <= <something>
```

Many things can be connected to a port, but right now, we only know about ports, so let us do the connection in `another_circuit` with them. So here is the new code of `another_circuit.rb`, please modify the file accordingly:

```
require_relative "my_circuit.rb"

system :another_circuit do
  input :clk, :rst
  [16].input :addr
  input :ce0, :ce1
  [8].input :data_in
  [8].output :data_out

  my_circuit(:my_circuit0)
  my_circuit(:my_circuit1)

  my_circuit0.clk <= clk
  my_circuit0.rst <= rst
  my_circuit0.addr <= addr
  my_circuit0.ce <= ce0
  my_circuit0.data_in <= data_in

  my_circuit1.clk <= clk
  my_circuit1.rst <= rst
  my_circuit1.addr <= addr
  my_circuit1.ce <= ce1
  my_circuit1.data_in <= data_in
end
```

If you are familiar with object-oriented or structured software programming, this code should be straightforward: the dot `.` operator is used to access a sub-element and in this case the ports of `my_circuit0` and `my_circuit1`. For example, the first connection line (line 10) connects the `clk` port of `another_circuit` to the one of `my_circuit0`, so that any data that goes through the former port will also go through the latter.

Now, the `data_out` ports are still not connected. It may be tempting to connect them like `data_in` as follows:

```
data_out <= circuit0.data_out
data_out <= circuit1.data_out
```


This will work indeed, but not the way you may think: in hardware, you cannot normally connect to one port several different objects. It is like assigning several values at the **same** time to a single variable. What will happen in HDLRuby, is that only the last statement will be kept, i.e., port `data_out` of `circuit0` will not be connected.

With such kind of cases, what we often want to do is to connect to `data_out` some computation result between the output of `circuit0` and `circuit1`. This is the opportunity to see another kind of construct that can be connected to a port: an expression. Like in software, an expression represents an arithmetic and logic computation. For example, let us consider the following connection:

```
data_out <= my_circuit0.data_out + my_circuit1.data_out
```

With this connection, the sum of the outputs `my_circuit0` and `my_circuit1` is transmitted through the output port `data_out` of `another_circuit`.

But when is this computation performed? This is a very good question: while in software, programs are executed one instruction after the other, in hardware, there is no such thing as the execution of instructions. The expression connected to `data_out` is not an instruction at all! It is a description of a part of the circuit that specifies that an adder (a circuit that does addition) must be instantiated with the output ports `data_out` of `my_circuit0` and `my_circuit1` connected to its inputs and its output connected to the output port `data_out` of `another_circuit`. The following figures show the schematic of this hardware portion:

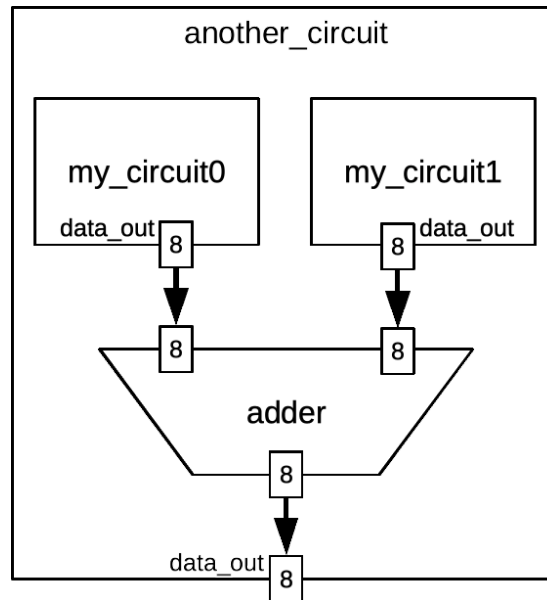

So, when this expression is executed? It is continuously executed, i.e., as soon as one of the outputs `data_out` of `my_circuit0` or `my_circuit1` changes, so does the output `data_out` of `another_circuit`.

For trying this new circuit, please update the code of `another_circuit.rb` as follows:

```

require_relative "my_circuit.rb"

system :another_circuit do
  input :clk, :rst
  [16].input :addr
  input :ce0, :ce1
  [8].input :data_in
  [8].output :data_out

  my_circuit(:my_circuit0)
  my_circuit(:my_circuit1)

  my_circuit0.clk <= clk
  my_circuit0.rst <= rst
  my_circuit0.addr <= addr
  my_circuit0.ce <= ce0
  my_circuit0.data_in <= data_in

  my_circuit1.clk <= clk
  my_circuit1.rst <= rst
  my_circuit1.addr <= addr
  my_circuit1.ce <= ce1
  my_circuit1.data_in <= data_in

  data_out <= my_circuit0.data_out + my_circuit1.data_out
end

```

Then, let us generate again Verilog HDL from it:

```
hdrcc --verilog another_circuit.rb work
```

Oh! If you get the following error message:

```

another_circuit.rb:15:in `block in <main>': undefined method `addr' for #
<HDLRuby::High::Namespace:<whatever number>>

```

Do not forget to replace the smiling face with `addr` in `my_circuit.rb`.

When the compile succeeds (no error message), two new files appear in `work`, namely `_v20_4.v` and `_v23_5.v`. Those are the new descriptions of `my_circuit`, they did not change, but since new hardware has been added their name changed. For the interesting part, let us open again `another_circuit.v`, the result should be as follows:

```
`timescale 1ps/1ps
```

```
module _v0_3( _v1_clk, _v2_rst, _v3_addr, _v4_ce0, _v5_ce1, _v6_data_in,
_v7_data_out );
    input _v1_clk;
    input _v2_rst;
    input [15:0] _v3_addr;
    input _v4_ce0;
    input _v5_ce1;
    input [7:0] _v6_data_in;
    output [7:0] _v7_data_out;
    wire _v8_0;
    wire _v9_1;
    wire [15:0] _v10_2;
    wire _v11_3;
    wire [7:0] _v12_4;
    wire _v13_5;
    wire _v14_6;
    wire [15:0] _v15_7;
    wire _v16_8;
    wire [7:0] _v17_9;
    wire [7:0] _v18_10;
    wire [7:0] _v19_11;

    _v20_4
    _v21_my_circuit0(._v1_clk(_v8_0),._v2_rst(_v9_1),._v3_addr(_v10_2),._v22_ce(_v11_3)
,._v6_data_in(_v12_4),._v7_data_out(_v18_10));
    _v23_5
    _v24_my_circuit1(._v1_clk(_v13_5),._v2_rst(_v14_6),._v3_addr(_v15_7),._v22_ce(_v16_
8),._v6_data_in(_v17_9),._v7_data_out(_v19_11));
    assign _v8_0 = _v1_clk;

    assign _v9_1 = _v2_rst;

    assign _v10_2 = _v3_addr;

    assign _v11_3 = _v4_ce0;

    assign _v12_4 = _v6_data_in;

    assign _v13_5 = _v1_clk;

    assign _v14_6 = _v2_rst;

    assign _v15_7 = _v3_addr;

    assign _v16_8 = _v5_ce1;

    assign _v17_9 = _v6_data_in;

    assign _v7_data_out = (_v18_10 + _v19_11);
```

`endmodule`

The code is starting to get complicated and seemed to be much different from the HDLRuby description than before. This is because this time, real syntactic limitations of Verilog HDL compared to HDLRuby have to be bypassed. Here, the limitation is that while in HDLRuby, ports can be connected wherever we want, in Verilog HDL, this must be done only while instantiating.

In fact, in HDLRuby too you can do the connection while instantiating, this is even recommended for better readability of the code. There are two ways to do so: by position (like for the arguments of a function call) or by name. Let us see both by editing again `another_circuit.rb` : please just replace both instantiation lines with the followings:

```
my_circuit(:my_circuit0).(clk,rst,addr,ce0,data_in,data_out)
my_circuit(:my_circuit1).(clk: clk, rst: rst, addr: addr, ce: ce1,
                          data_in: data_in, data_out: data_out)
```

The instantiation for `my_circuit0` does the connection by position, that is to say, that each port given between the second parenthesis is connected in the order of declaration of in ports of `my_circuit.rb` . For `my_circuit1P` the connection is done by name: then syntax `:` connects ports named name of the instance of `my_circuit` to something . For example `clk: clk` connects port `clk` of `my_circuit0` to port `clk` of `another_circuit``.

That's all for this section!

Now you know:

- How to declare a new circuit with its name and ports in HDLRuby.
- How to check it with `hdrcc`.
- How to convert it to Verilog HDL.
- How to reuse it into another circuit.
- And even, how to describe the computation of some expressions and connect them to an output port.

But you still do not know: how to describe more complex computations, e.g., controls, and how to simulate a circuit. Let us start slowly (from the software person's point of view) with how to describe an algorithm the simple way in HDLRuby.

3. How to describe an algorithm to be implemented by a circuit

In this section we will see:

- [How to handle values in a circuit.](#)
- [How to describe an algorithm that a circuit can implement.](#)

3.1. How to handle values in a circuit

In software, value handling looks straightforward enough: they are computed with expressions and are stored into variables. In hardware it is slightly different since two kinds of components handle values: the wires and the

storage components:

- The wires are abstractions of physical wires or sets of wires that transmit data to the hardware component they are connected to. A wire cannot hold a value: if a component drives a value to a wire, this wire takes this value, and it will last as soon as this drive stops.
- The storage components are abstractions of registers or memories that can hold values. Depending on how they are described, the value they hold can be changed on specific events like the rising edge of a clock. Hence, the storages component are closer to the software variable than the wires.

With HDL like Verilog HDL, there is a real distinction between wires and storage components. However, with other HDL like VHDL, or here with HDLRuby, both are abstracted by a single concept: the signal. Specifically, when a signal is only driven on a given event, it becomes a storage element, otherwise, it will remain a wire.

Note: one may ask what about the `variable` construct in VHDL: those are syntactic intermediates used for simplifying the descriptions. HDLRuby also supports such a `variable` construct, but extended to hold anything and not only values as explained in the section about [mixing Ruby and HDLRuby](#).

In HDLRuby, there are three kinds of signals: the input ports, the output ports, the inout ports, and the inner signals. The first three kinds of signals have already been described in the section about declaring a [circuit](#). The inner signals can be used inside a circuit and are usually used as an intermediate for internal computations. They are declared like the ports, but using `inner` instead of `input`, `output`, or `inout`. For example, the following code declares a module named `a_circuit` with two 1-bit inputs, one 8-bit output, and one 4-bit inner signal.

```
system(:a_circuit) do
  input :u, :v
  [8].output :z

  [4].inner :sig
end
```

Note: the inner signals as well as the ports can be declared anywhere within the body of a module. It is however recommended to declare the ports at the beginning, and the inner signal when relevant, e.g., it may not be a good idea to declare a signal at the beginning of a circuit description if it is only used at the end.

What about the data types?

For now, we only used positive integer values, e.g., `[8].inner` declares an 8-bit positive integer. To tell the truth, `[8]` is not the designation of the 8-bit positive integer data type, but a syntactic sugar that stands for: `bit[8]`. As a general rule, in HDLRuby, the designation of a data type is as follows:

```
<base>[<range>]
```

Where `base` is another data type and `range` describes the range of indexes used for accessing its elements individually. In addition, there are three root data types used for building all the other ones:

- `bit` : for boolean, or 1-bit unsigned values, i.e., the only possible values are 0 and 1.
- `signed` : for 1-bit signed values in 2's complement, i.e., the only possible values are 0 and -1.
- `float` : for 1-bit floating point values, but, **WARNING:** this data type is not supported yet!

For example, a 32-bit input signed integer signal and an inner array of eight 24-bit using integers are declared as follows respectively:

```
signed[32].input :sig
bit[24][8].inner :ar
```

Unfortunately, the following is not valid:

```
[24][8].inner :ar
```

This is because it conflicts with other constructs in the language.

When the code above is declared, you can access one element of array `ar` using the brackets like before, e.g., its first element is `ar[0]`, its second one `ar[1]`, and so on. But you can also access its last element as follows:

`ar[-1]`, its element before the last one as follows `ar[-2]`, and so on. Moreover, since an integer is just an array of bits, it is possible to access its bits individually in the same way. For example, accessing the first bit of the last element of `ar` can be done as follows: `ar[-1][0]`.

But compared to the software you can do even more than that: you can also access to sub-range of elements of a signal. For example, assigning bits from index 4 to 27 of signal `sig` to element 1 of `are` can be written as follows using *range*:

```
sig <= ar[1][27..4]
```

A range is noted as follows: `<start value>..<end value>`, and indicates respectively the value of the first and the last indexes. Convenient, is not it? But wait... Why `27..4` and not `4..27`?

Let us talk about endianness.

If you are familiar with hardware or with low-level software, you may be aware of this topic. There is two possible way for reading a value or the content of an array: from the most significant bit or index to the least significant one (big-endian) and the opposite (little-endian). Since big-endian is more natural for reading numbers it is the default mode in HDL, including HDLRuby. However, for an array, software programming usually does the opposite. In HDLRuby, using little-endian instead of big-endian is declared by using a negative number for the size instead of a positive one.

As a general rule, code will be much easier to understand if integer values are big-endian and the array accesses little-endian. That is to say that the following declaration is the best for `ar`:

```
bit[24][-8].inner :ar
```

One last thing: it is also possible to set the numbering of each bit of a signal using again a *range* instead of an integer indicating the size. For example, with the following declaration, `a` is an 8-bit big-endian integer with its bits numbered from 0 to 7, and `b` is a 9-bit little-endian integer with its bits numbered from 1 to 9:

```
[7..0].inner :a
[1..9].inner :b
```

But what happens when we make operations between signals of different types?

About casting and auto-casting

First, like in software, you can convert the type of a signal using the cast operator `as`. For example, in the following code, the result of a 16-bit unsigned addition is performed between the 8-bit signal `x` converted to 16-bit and the 16-bit signal `y`:

```
[8].inner :x
[16].inner :y, :z

<some code>

z <= x.as(bit[16]) + y
```

However, if you do not use the cast operator, HDLRuby will do it automatically for you and cast the operands the largest of their types. That is to say that for the following code the result is identical to the previous one:

```
[8].inner :x
[16].inner :y, :z

<some code>

z <= x + y
```

This rule means that for the following code, `z` will have the result of an 8-bit addition since both operands `x` and `y` are 8-bit:

```
[8].inner :x, :y
[16].inner :z

<some code>

z <= x + y
```

If you want a 16-bit addition, you must add a cast to at least of the operands, e.g.:

```
[8].inner :x, :y
[16].inner :z

<some code>

z <= x.as(bit[16]) + y
```

These explanations about data types may have been not so fun, but we should better get over with them first so that now we can start the real fun with actual "programming"...

Note: "programming" is put between quotes because this is not programming since there is no program, but instead a description of a physical circuit.

3.2. How to describe an algorithm that a circuit can implement

So now you know how to declare a circuit, use it, connect it, and declare variable-like constructs that are called signals. We will see in a very short while that signals are definitive **not** software variables, but let us go on with the illusion for a little while and see how you can describe an algorithm in HDLRuby. As a side note, the features

described in this section are unique to HDLRuby so do not expect to be able to do the same with Verilog HDL or VHDL.

With software languages, when you want to describe an algorithm you use assignment statements and control constructs like `if`, `for`, or `while`. If you know higher-level languages like `Java` or `Ruby` you may also use design patterns like `iterators` (or `enumerators`). You can do the same in HDLRuby with constructs called *sequencers*. At first glance, a sequencer can be seen as the description of a hardware component implementing a software algorithm. Hence, a sequencer may look like a processor, but there are differences:

- It is not possible to change the algorithm implemented by a sequencer (you cannot "load" a new program).
- A sequencer starts execution according to a given start signal, and from there advances execution of each cycle of a given clock.
- You have control at the clock cycle level of the algorithm, and incidentally, a sequencer is much more efficient than a processor executing a program.

This section will explain the following about sequencers:

- [How to declare and control a sequencer.](#)
- [How to write a structured programming algorithm in a sequencer.](#)
- [How to use enumerators in a sequencer.](#)
- [What happens when there are several sequencers?](#)

3.2.1 How to declare and control a sequencer

As said in the previous section, a sequencer advances execution according to a clock and starts execution according to a start signal. We discuss later [clocks](#), but for now, you just need to know that it is a single-bit signal that alternates from 0 to 1, and it is the transition from 0 to 1, or from 1 to 0 of this signal that will make a sequencer progress execution. Let us see two examples of sequencers to understand better:

```
system :the_counter do
  inner :clk, :start

  sequencer(clk,start) do
  end
end
```

In the code above, a system containing one sequencer is described. The sequencer will be controlled by the start signal `start` and clock signal `clk`, which means that:

- it will advance execution every time `clk` switches from 0 to 1, we call such an event a *positive edge* of `clk`;
- it will start when signal `start` switches from 1 to 0, we call such an event a *negative edge* of `start`.

Why a positive edge for `clk` and a negative one for `start`? It does not matter much, and you can specify the edges you want using the `posedge` and `negedge` methods. For example, the following sequencer advances execution on a negative edge of `clk` and starts on a positive edge of `start`:

```
sequencer(clk.negedge,start.posedge) { }
```

Note: the curly brackets used here are equivalent to the `do` and `end` keywords we used until now.

WARNING: there is a caveat though, since a sequencer advances execution according to a clock signal, it will not be able to start properly unless the start signal is strictly slower than the clock. In practice, the start signal should stay at 0 in case of posedge or at 1 in case of negedge longer than one clock cycle.

But now, what will this sequencer do? Nothing right now since its body is empty. So let us start small and make it count the number of a few clock cycles:

```
system :the_counter do
  inner :clk, :start
  [8].inner :count

  sequencer(clk,start) do
    count <= 0
    step
    count <= count + 1
    step
    count <= count + 1
    step
    count <= count + 1
  end
end
```

The first line of the body of the counter looks like the connection of ports we described [previously](#). However it is inside the body of a sequencer and will therefore be *executed* by it, that is to say, before this statement is executed, `count` may not be 0, and after, it may have another value. More generally:

- Every assignment statement outside sequencers (and later behavior) are connections: the signal will *always* and *continuously* have the value that is assigned to them. The reciprocal is also true: the assigned values will *always* and *con continuously* have the value of the signal.
- The other assignment statements, e.g., the ones inside a sequencer, are called *transmission* in HDLRuby and happen only when *executed*.

In our example, the count is there for set to 0 when the sequencer starts execution. But before that... no one knows the value of count, it is said to be *undefined*.

Just after this initial line, there is the `step` keyword. There we go from the software world to the hardware one: this keyword indicates that the sequencer ends execution here until the next clock cycle. Looking at the subsequent line you may understand why we waited: this line increases the value of `count` by one, i.e., the sequencer counted one clock cycle. Again, a `step` is inserted, and `count` is increased, and so on, so that this is indeed the code of a sequencer that counts the clock cycles. However the code ends after 3 clock cycles, and like with software, when the code of a sequencer is over, it stops execution.

This may look abstract, so let us try to simulate this circuit. For that purpose, write the code into a file named `the_counter.rb` (for example) and try the following command that will simulate the circuit:

```
hdrcc --sim the_counter.rb the_counter
```

If everything was all right the following text will appear:

```
__:T:0:::2: 000
```

It indicates that a signal named `__ : T:0::2` has been initialized to 0 (000), and that's all... Why is that, and why *only* that? First, this signal with a strange name has been generated by HDLRuby for the internal processing of the sequencer and is required to be initialized to 0. So, ok, the simulation did some initializations but did not seem to do any execution. This is because we did not give any description of the physical environment of the circuit, and especially, we did not say that the clock and the start signal need to change value. For describing the behavior of the environment of a circuit, we use a construct called in HDLRuby the *timed behavior*. They are somewhat close to sequencers but are not controlled by a clock signal but by physical time. So let us add the following code just after the sequencer (but still inside the module `the_counter` :

```

timed do
  clk <= 0
  start <= 0
  !10.ns
  clk <= 1
  !10.ns
  clk <= 0
  start <= 1
  !10.ns
  clk <= 1
  !10.ns
  clk <= 0
  start <= 0
  !10.ns
  clk <= 1
  !10.ns
  clk <= 0
  !10.ns
  clk <= 1
  !10.ns
  clk <= 0
  !10.ns
  clk <= 1
  !10.ns
  clk <= 0
  !10.ns
  clk <= 1
  !10.ns
  clk <= 0
  !10.ns
  clk <= 1
  !10.ns
  clk <= 0
  !10.ns
  clk <= 1
  !10.ns
end

```

Sorry, this code is a little bit long... Did you add it to the file `the_counter.rb` ? now please try again the simulation command:

```
hdrcc --sim the_counter.rb the_counter
```

You should have the following result:

```

__T:0::2: 000
__T:0::clk: 0
__T:0::start: 0
# 10000ps
__T:0::clk: 1
__T:0::1: 000
# 20000ps
__T:0::clk: 0
__T:0::start: 1
# 30000ps
__T:0::clk: 1
__T:0::2: 001
# 40000ps
__T:0::start: 0
__T:0::clk: 0
# 50000ps
__T:0::clk: 1
__T:0::1: 001
__T:0::count: 00000000
__T:0::2: 010
# 60000ps
__T:0::clk: 0
# 70000ps
__T:0::clk: 1
__T:0::1: 010
__T:0::count: 00000001
__T:0::2: 011
# 80000ps
__T:0::clk: 0
# 90000ps
__T:0::clk: 1
__T:0::1: 011
__T:0::count: 00000010
__T:0::2: 100
# 100000ps
__T:0::clk: 0
# 110000ps
__T:0::clk: 1
__T:0::1: 100
__T:0::count: 00000011
__T:0::2: 101
# 120000ps
__T:0::clk: 0
# 130000ps
__T:0::clk: 1
__T:0::1: 101
__T:0::2: 000
# 140000ps

```

If you look at the last line of the simulation result you should have `# 140000ps` , which means that final the simulation time was 140000 pico seconds (140 nanoseconds). If you look at the result in totality, you will see an alternation of signal names followed by a value in binary (e.g., `__T:0::clk: 1` for the `clk` signal is 1) and an indication of the time of the simulation. The names look indeed messy, but please only focus on the last part of the name: that will be the name of the signal you defined in your HDLRuby file. You will also notice some signals that you did not declare (e.g., `__T:0::1` and `__T:0::2` , but those are only signals generated by HDLRuby.

Now, let us see what happened, and what was the meaning of the `timed` construct we added. As explained before, `timed` constructs are like sequencers, but controlled by physical time instead of a clock signal. Inside, you can put assignments but also statements that will advance the time. For instance: `!10.ns` is a statement that will advance time by 10 nanoseconds (i.e., 10000 picoseconds). Hence, with such a construct you can tell that

some signal will take a given value at a given time. For this example, it is enough to tell how the `clk` and `start` signal change over time to make the sequencer run by itself. Hence, the `clk` signal is made to switch from 0 to 1 then from 1 to 0 every 10 nanoseconds, which simulates a 50 MHz clock, and the `start` signal is set to 1 and then to 0 so that the sequencer starts execution. The first thing it does is set `counter` to 0, and then the following cycles this counter is increased until its execution completes. Even when the sequencer completes execution, the simulation goes on though, until the timed behavior also completes.

WARNING: in HDLRuby, everything is synthesizable, i.e., can be turned into a real circuit, apart from the timed behaviors. These constructs are there for simulating the physical environment of a circuit for testing it.


Ugh! The simulation result is ugly!

Indeed, the text output of the simulator quickly becomes hard to read, and therefore we highly recommend generating a graphical one using the following command:

```
hdrcc --sim --vcd the_counter.rb the_counter
```

The new option `--vcd` make the simulator produce a *Value Change Dump* file (VCD) that can be visualized graphically by many HW design tools. If you do not have any such you can get [GTKWave](#) which is under GNU General Public License v2.0.

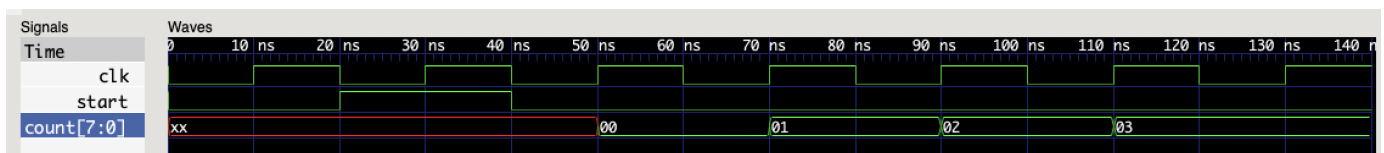The resulting vcd file can be found in the `the_counter` directory with the name `hruby_simulator.vcd`. If you open it and select the `clk`, `start`, and `counter` signals you will see something like the following picture:



Such a graph is called a time chart and displays the evolution of signals with time on the X-axis. You can see that `clk` is indeed alternating from 0 to 1, and that `start` is set to 1 for one clock cycle only. After this later signal becomes 0 again, the sequencer starts. This can be verified by looking at the value of `counter`: at first, it is undefined, that it is set to 0, then increased by 1 at each clock cycle until it reaches 3.

So now, you know:

- How to describe an algorithm in HDLRuby.
- How to simulate it.
- How to display a cool graph showing the simulation results (maybe?)

Hum, the *algorithm* part is quite limited, and the timed behaviors seem to be real pains to write. So let us see how to do better in the following section.

3.2.2. How to write a structured programming algorithm in a sequencer

Now, when we speak about algorithms, we often think about software constructs like `if` for conditional execution and `for` for loops. Unfortunately, in HW design this is usually not that simple at all... But for HDLRuby sequencers it is indeed that simple: all these control statements are supported without any limitation. The only thing you have to be careful about is their name: to avoid confusion with the Ruby language, their names are all prefixed with an `s` (for *sequencer*), e.g, you have to use `sif` for doing an *if*.

In detail here is a list of the control statements you can use within a sequencer:

- `sif(<condition>) <block>` : executes `block` if `condition` is true (i.e., different from 0).
- `selsif(<condition>) <block>` : executes `block` if the previous `sif` or `selsif` condition is not met and if the current condition is met.
- `selse <block>` : executes `block` if the condition of the previous `sif` is false (i.e., equals 0). It is also used for giving the default block for the `scase` statement (see below).
- `scase(<choice>)` : initialize a multiple case statement.
- `swhen(<value>) <block>` : executes `block` if `value` is equal to `choice` in the previous `scase` statement.
- `sloop <block>` : loop infinitely repeating the execution of `block` (yes, like Ruby, if you want to do an infinite loop, do it explicitly, no semantically absurd `while(TRUE)` even if you can).
- `swhile(<condition>) <block>` : repeat the execution of `block` as long as `condition` is true.
- `sfor(<enumerable>) <block>` : executes `block` on each element of `enumerable` .
- `sbreak` : ends the current loop (even if it is a `sloop`).
- `scontinue` : ends the current iteration.

IMPORTANT: each control statement requires one clock cycle for each branch they perform, independently of what their block contains. For example, in the following code, the value of `y` will be set one cycle after `x` is set to 0, and one cycle before `z` is set to 1.

```
x <= 0
sif(~x) { y <= 2 }
z <= 1
```

Let us see the details about these constructs with a few examples. First, let us make a circuit that computes the factorial of an input value when asked for:

```

system :fact do
  input :clk, :start, :req
  [5].input :data_in
  output :ack
  [32].output :data_out

  [4].inner :val
  [24].inner :res

  sequencer(clk,start) do
    sloop do
      ack <= 0
      swwhile(req != 1)
      val <= data_in
      res <= 1
      swwhile(val>1) do
        res <= res*val
        val <= val - 1
      end
      data_out <= res
      ack <= 1
    end
  end
end

```

The code is more complex than what we have seen up to now, so let us study it progressively:

- The circuit is named `fact` (for factorial).
- It has four inputs:
 - `clk` and `start` : the signals that controls the execution of the sequencer (nothing new here).
 - `req` : the signal that will ask for a factorial computation (*req* for require).
 - `data_in` : the signal that will provide the input value. It is a 4-bit unsigned integer.
- It has two outputs:
 - `ack` : the signal that will tell that the current computation of factorial is over. Such a signal is necessary for the environment to know if the output result is valid or not since the computation time of a factorial depends on the input value.
 - `data_out` : the signal that will hold the computation result. It is a 24-bit unsigned integer, much larger than the input, but we are computing factorials here! (this is not enough yet: $15! = 1307674368000$ which requires 41 bits... But 24-bit was the largest that could fit in the picture of the time chart that is shown after.)
- The sequencer includes an infinite loop (`sloop`) so that it does not stop after one computation. Within this loop:
 - It first sets `ack` to 0 to tell that currently, its output is not valid (no computation is done yet).
 - Then it waits for a request, i.e., it waits for that signal `req` is 1. This loop (`swwhile(req != 1)`) does not have any block to execute, it will therefore loop without doing anything.

- When `req` becomes 1, it loads the input value into an internal temporary signal (`val`) and initializes the computed value (`res`) to one.
- Finally, it loops by multiplying `res` by `val` and decreasing `val` until 1 is reached before assigning the computation result to `data_out` and setting `ack` to 1 for telling the computation is over.

Does it work?

Now let us simulate this circuit. For that, you now know that we must describe the environment using a `timed` behavior. But this time, let us do this properly by putting the description of the environment in a different module to separate the circuit description from the simulation: please write in a file named `direction.rb` the code of module `direction` then the following code:

```
system :fact_bench do
  inner :clk, :start, :req, :ack
  [4].inner :x
  [24].inner :z

  fact(:factI).(clk,start,req,x,ack,z)

  def clk!
    clk <= 0
    !10.ns
    clk <= 1
    !10.ns
  end

  timed do
    start <= 0
    !10.ns
    clk!
    start <= 1
    req <= 0
    clk!
    start <= 0
    repeat(2) do
      clk!
    end
    req <= 1
    x <= 10
    clk!
    req <= 0
    repeat(20) do
      clk!
    end
  end
end
```

This module introduces the `repeat` construct. It can be used within timed behavior only and have the following syntax:


```
repeat(<number>) <block>
```

It executes the `block` `number` times with the number of iterations as an argument.

WARNING: the `repeat` construct cannot be used outside a timed behavior. Inside a sequencer, you can use instead `swhile` or `sfor`.

There is also a new kind of command in the timed behavior: `clk!`. This is not a command, but a Ruby function defined just before with the `def` block. If you are not familiar with Ruby, `def` is used for defining a new function (actually a method), also, it is not necessary to put parenthesis when calling a function. Hence, `clk!` is simply the call of this previously defined function (in Ruby, function names can terminate with characters like `!` or `?`). If you look at the body of this function, you will see not plain Ruby code, but again HDLRuby code:


```
clk <= 0
!10.ns
clk <= 1
!10.ns
```

IMPORTANT: indeed, as said when presenting HDLRuby, this language is implemented on top of the Ruby language, and is fully compatible with it: you can write any Ruby code within HDLRuby constructs (e.g., `def`), and you can write HDLRuby code within Ruby constructs. However, there is an important difference: Ruby code is executed at compile time (i.e., when `hdrcc` runs) and does not produce any hardware, whereas HDLRuby code is the description of the hardware that will be produced and will be then executed either through simulation or after production physically. Then, what calling `clk!` does is paste the HDLRuby code in its body. Here it is used to shorten the code: instead of setting each time the clock to 0, advance time then setting it to 1, writing `clk!` is enough to obtain the same result. It is from this capability to mix Ruby and HDLRuby that comes to the *metaprogrammability* of HDLRuby.

Finally, when you simulate with the following command:

```
hdrcc --sim --vcd direction.rb direction
```

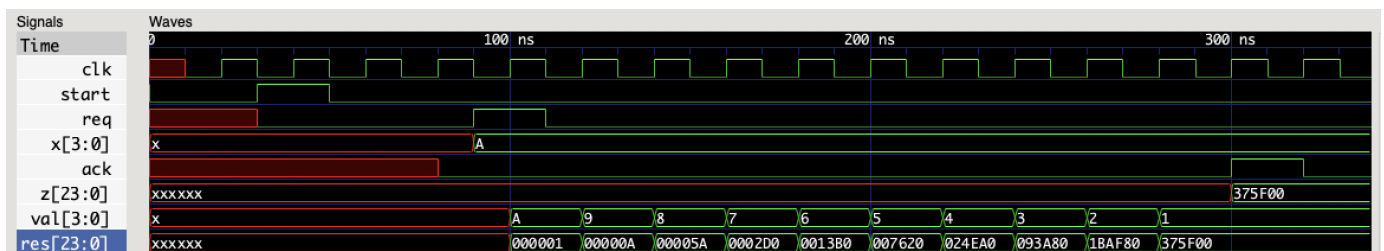You should obtain the following kind of resulting VCD file:



If you are familiar with the software, the index access `previous[1]` looks like array accesses. And it is indeed the same meaning in hardware, however, contrary to software, integer values are seen as an array of bits. This is also the reason why since the beginning of this tutorial, values are declared somewhat like arrays, e.g., an 8-bit signal named `x` is declared as follows: `[8].inner :x`. And what if one wants to declare an array of four 8-bit values? Then, use again the brackets, e.g.:

```
bit[8][4].inner :ar
```

Now about `sfor`

With a `for` statement you may expect something like C with the definition of an index, its initialization, and its increment. However, the `sfor` of HDLRuby is simpler: it only takes as argument an enumerable object and will iterate on each of its elements. An enumerable object is any Ruby enumerable object as well as any signal. For example, the following circuit outputs bit by bit the content of a 32-bit input value:

```
system :serializer do
  input :clk, :start, :req
  [32].input :data_in
  output :tx, :data_out

  sequencer(clk, start) do
    tx <= 0
    data_out <= 0
    sloop do
      sif(req) do
        tx <= 1
        sfor(data_in) do |b|
          data_out <= b
        end
        tx <= 0
        data_out <= 0
      end
    end
  end
end
```

This circuit takes as input `data_in` and sends its content bit by bit to `data_out` when `req` is set to 1. In detail, it first indicates the beginning of the transmission by setting `tx` to 1, then from the next clock cycle will send one bit of `data_in` per clock cycle. When the transmission is over, it sets `tx` to 0 again. There are a few more details to unwrap:

- By default both `tx` and `data_out` are set to 0, this is done at the beginning of the sequencer but also just after the `sfor`.
- `tx` is set to 1 just before the `sfor` loop, i.e., one cycle before the actual transmission. As said in the description of the [control statements](#), each of them requires one clock cycle before branching.

Even if for this case, it is not the clearer way, the `for` loop could also have been implemented using an index as follows:

```
sfor(0..31) do |i|
  data_out <= data_in[i]
end
```

However, the advantage of the first version of the code is that it is still valid when the data type of `data_in` is changed whereas the second version must be rewritten to adjust the range of the index.

If you want, you can try this serializer, you need to add a module representing the environment. For example:

```

system :serializer_bench do
  inner :clk, :start, :req, :tx
  [8].inner :x
  inner :z

  serializer(:serializerI).(clk,start,req,x,tx,z)

  def clk!
    clk <= 0
    !10.ns
    clk <= 1
    !10.ns
  end

  timed do
    start <= 0
    !10.ns
    clk!
    start <= 1
    req <= 0
    clk!
    start <= 0
    repeat(2) do
      clk!
    end
    req <= 1
    x <= _hAB
    clk!
    req <= 0
    repeat(16) do
      clk!
    end
  end
end
end


```

There is a new notation: `_hAB`, this is used for representing fixed bit-width hexadecimal. Since there are two digits, it is an 8-bit value. You can also use binary representations as follows: `_b10101011`.

When everything is put in a file named: `serializer.rb` and simulated as follows:

```
hdrcc --sim --vcd serializer.rb serializer
```

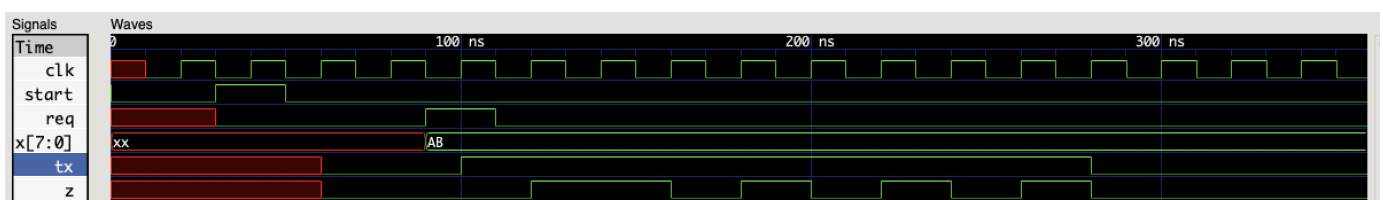You should obtain the following time chart:



So now, you know:

- How to describe fully fledged algorithms with sequencers.

Also, if you are not familiar with languages like Ruby or Python, the `sfor` may look great compared to what C can provide. But this is just the beginning, HDLRuby can do even better than that.

3.2.3. How to use enumerators in a sequencer

If you are familiar with Ruby, you may know about enumerators: there are objects used for processing iteratively several elements of objects. The HDLRuby's sequencer provides the same concept: it is possible to build hardware enumerators for any enumerable objects, that will run like Ruby's.

We strongly recommend before going on with this tutorial study the Ruby enumerable and enumerators. Indeed, HDLRuby enumerators and enumerable objects reproduce the functionalities of Ruby, we will only point out what is specific to hardware.

First, what is an enumerable?

So, enumerators iterate over enumerable, but what is it? In HDLRuby, an enumerable is either a Ruby enumerable object, an enumerator (Ruby or HDLRuby), or a signal of any type. If the signal is an array, the iteration will be over its elements, if it is a number, it will be done over its bits. For example, `0..2` is an enumerable including 0, 1, and 2 as elements, `[3,6,7]` is one including 3, 6, and 7, and the following signal `sig` include 0, 1, 1, 0, 1, 1, 1, 0:

```
[8].inner sig: _b01110110
```

Let us build HDLRuby enumerators.

Like Ruby builds enumerators using the `each` method and its derivatives (`each_with_index` and so on,) HDLRuby uses the `seach` method to build its enumerator. For example, an enumerator over the bits of signal `sig` will be built as follows: `sig.seach`, and if you want an enumerator with index, just like Ruby: `sig.seach_with_index`, and so on. Then, an enumerator can be executed when create by providing the block that will be applied on each element like in ruby, or executed later using the `seach` method again. E.g., the following sequencer code first sums the bits of signal `sig` at once, then do it again later with another enumerator:

```
input :clk, :start

[8].inner sig: _b01110110
[4].inner num0, :num1

sequencer(clk,start) do
  another_enum = sig.seach
  num0 <= 0
  num1 <= 0
  sig.seach {|b| num0 <= num0 + b }
  sig <= _hCD
  another_enum.seach {|b| num1 <= num1 + b }
end
```

That's all that we will explain here, the remaining is exactly like Ruby. Moreover, almost all the methods related to enumerable and enumerator have been reimplemented in HDLRuby using the prefix `s`, so please refer to the main documentation of HDLRuby about [enumerators](#) for details. Let us just see a few examples:

- Count the number of 1 bit of a signal -- again -- but within an infinite loop, and with a much shorter code using the HDLRuby version of the Ruby enumerator method `reduce` :

```
input :clk,:start
[8].input :sin
[4].output :sout

sequencer(clk,start) do
  sloop do
    sout <= sin.sreduce(_h0,&:+)
  end
end
```

Here are a couple of remarks about this code:

- You may have noticed that the initial value of `reduce` is set to a 4-bit 0 (`_h0` , since a hexadecimal digit is 4-bit). If this value is not set, the data type of the elements will be used for the additions, in this case, 1-bit (and a 1-bit addition is actually an exclusive or).
- While the count of the bits is a single-line statement, it is executed like a usual sequencer loop and therefore requires 8 clock cycles for completing.
- Fills array `ar` from input `sin` one byte per cycle then sort it and outputs its content one byte per cycle.

```
input :clk,:start
[8].input :sin
[8].output :sout

bit[8][-16].inner :ar

sequencer(clk,start) do
  16.times { |i| ar[i] <= sin }
  ar.sort
  16.times { |i| sout <= ar[i] }
end
```

In this example, `8.times` generate an enumerator over the `0..7` range, and is a way to build an enumerator from an integer value.

- Apply a 4-point FIR filter over an array obtained from input signal `sin` with 0-padding at the beginning and output the result to `sout`

```

input :clk,:start
[8].input :sin
[8].output :sout

bit[8][-4].inner coefs: [_h01,_h05,_h0A,_hFE]
bit[8][-16].inner : ar

sequencer(clk,start) do
  16.stime { |i| ar[i] <= sin }
  sout <= ([_h00]*3).seach + ar.seach).seach_slice(4).sreduce(_h00) do |a,b,c,d|
    a*coefs[0] + b * coefs[1] + c * coefs[2] + d * coefs[3]
  end
end
end

```

In this example, `[_h00]*3` builds an array of three 8-bit zeros for the padding, `seach` creates the iterators over the padding, and the array and their sum create a global iterator over them all. `seach_slice` and `sreduce` work the same way their Ruby equivalent `each_slice` and `reduce` work.

Create your enumerator.

The method `seach` and its derivatives make it possible to iterate over signals or other enumerable objects. But you can also create your enumerator that can iterate on whatever you want and the way you want. For that purpose, please use the following command:

```
<variable> = senumerator(<element type>, <number of elements>) <block>
```

Where `block` is a block of sequencer code for accessing an element by index. For example, the following defines the enumerator named `enum0` enumerating over the 100 first square numbers in 32-bit:

```
enum0 = senumerator(bit[32],100) { |i| i*i }
```

It is also possible to put a sequencer control statement in the access block, for example, the following enumerator accesses each bit of signal `x` waiting for 2 cycles between each access:

```

[128].input :x
enum1 = senumerator(bit,x.width) do |i|
  step
  step
  x[i]
end

```

Now you know:

- You create enumerators.
- How to use enumerators for easily building complex algorithms.
- How to create your enumerators.

And with that, you can build sequential hardware almost as easily as software. But why bother? Simply because the performance of the resulting hardware is much better than that of software, at least in terms of energy and/or power consumption.

But this is not all: contrary to software, hardware is inherently parallel, a property that has not been considered at all yet. From now on, that will be the main topic of this tutorial. We will start slowly by studying what happens when there are several sequencers.

3.2.4. What happens when there are several sequencers?

General considerations.

You can have as many sequencers as you want in a module, and of course, you can have as many modules as you want in a circuit description. In total, all these sequencers will run independently of each other and in parallel. Furthermore, these parallel sequencers can be controlled by the same clock and start signals or by different ones.

As long as the sequencers do not access the same signals, they will not interfere with each other and what has been explained up to now is enough. However, it is common that the various parts of a circuit cooperate, and therefore exchange information, i.e., access common signals. There are two ways to handle access to the same signal from several sequencers...

The easy way: stick to simple rules

There is a simple rule in hardware design to avoid any trouble when accessing a signal:

A signal can be read from anywhere at any time, but only one component (e.g., a port connection or a sequencer) can write to a given signal.

This rule is not absolute as you will see in the **hard way** to access signals, but it has the advantage of not requiring any additional hardware construct to be implementable. Hence, we do recommend following this rule as much as possible.

Let us see an example for understanding how several sequencers can interact the **easy way**. First, let us consider a sequencer that increases periodically a value and sends it to another sequencer that will count the number of bits of this value and tells the first one to proceed with the increase:

```

system :bit_pong do
  inner :clk, :start
  inner :req, :ack
  [4].inner :value
  [3].inner :count

  sequencer(clk, start) do
    req <= 0
    value <= 0
    sloop do
      req <= 1
      swhile(ack != 1)
      value <= value + 1
      req <= 0
    end
  end

  sequencer(clk, start) do
    ack <= 0
    count <= 0
    sloop do
      ack <= 0
      swhile(req != 1)
      count <= value.sreduce(_h0, :+)
      ack <= 1
    end
  end

  def clk!
    !10.ns
    clk <= 1
    !10.ns
    clk <= 0
  end

  timed do
    clk <= 0
    start <= 0
    clk!
    start <= 1
    clk!
    start <= 0
    repeat(100) { clk! }
  end


end
end

```

If you write this code in a file named `bit_pong.rb` and simulate it as follows:

```
hdrcc --sim --vcd bit_pong.rb bit_pong
```

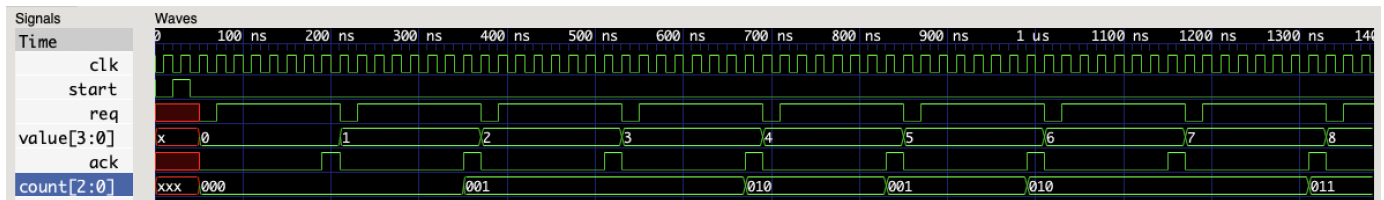
You will obtain the following kind of time chart:



You may notice a detail that is crucial in hardware: the increase of `value` by the first sequencer starts not when `ack` becomes 1, but the next clock cycle. This is the second important rule in hardware design:

When a signal is read in a clock-synchronized component (e.g., a sequencer), the real value is not the value of the signal at this exact instant, but the one it has a little while before. This is because hardware implementation of signals takes physical time to propagate.

With these simple rules, one can easily and efficiently implement a large range of applications. But a few cases do require several components (e.g., sequencers) to write to the same signal. For example, when a resource must be shared among several components. Let us see what can be done in such kinds of cases.

The hard way: arbitrating between writes to signals

The problem when several components write to the same signal is handling the cases where different values are assigned at the *same* time. This requires extra arbitration circuitry that must be described by the designer or generated by the synthesis tool. Since there is no *good* way of arbitrating, the first option is the most common, but with HDLRuby's sequencer, there is an intermediate solution that does not require designing a new circuit but still lets the designer control the arbitration. It is this approach that is explained here, for the design from scratch of an arbitration please consult tutorials about advanced RTL design.

The hard way but not so much: shared signals

The HDLRuby sequencer supports another kind of signal called the *shared signals*. They are inner signals of a module that can be written to by any number of sequencers without causing any trouble. They are declared like any other inner signals, but using the `shared` keyword instead of `inner`. For example, a shared 8-bit signed signal named `sh` can be declared as follows:

```
signed[8].shared :sh
```

After being declared, shared signals can be used exactly like any other inner signals, but without any restriction when written within a sequencer.

But what about the arbitration?

By default, the arbitration when writing to a shared signal is blunt: the first declared sequencer that writes to this signal is **the only one** that changes its value. The other sequencers' writes are simply ignored. For example, in the following, code, the value of `sh` is 55, whatever the second sequencer does:

```

signed[8].shared :sh

sequencer(clk,start) do
  sh <= 55
end

sequencer(clk,start) do
  100.times { |i| sh <= i }
end

```

This is not so useful that way, but you can control that by setting which sequencer has exclusive using the `select` method of a shared signal. For example, in the following code, the first sequencer first writes 55 to `sh` but then gives access to the second one:

```

signal[8].shared :sh

sequencer(clk,start) do
  sh <= 55
  sh.select <= 1
end

sequencer(clk,start) do
  100.times { |i| sh <= i }
end

```

With this code, the value of `sh` will be at each clock: 55, 1, 2, 3,...

This is simple enough, right? However, there is a limitation: only one sequencer can access to the `select` of a shared signal... Otherwise, another layer of arbitration is required and we are back to the beginning. Often, this is all right, but sometimes, complex arbitration between several sequencers and several signals makes things messy.

Enter the global arbiters

So, you have multiple sequencers fighting with each other for accessing several shared signals, what to do? You need a global arbiter that will decide for everyone. The sequencer library provides such a module, named `arbiter` that is instantiated like any module. However, it does not have any specific port, instead, it must be connected to the shared signals it will arbitrate. For example, an arbiter named `arb01` controlling shared signals `sh0` and `sh1` can be declared as follows:

```
arbiter(:arb01).(sh0,sh1)
```

Then, when a sequencer wants to write to either `sh0` or `sh1` it must ask the acquire the right by sending 1 to the arbiter, and when the access is done, it must release the right by sending 0 so that it does not monopolize the signal. For example, the following sequencers write in turn to the 2-bit shared signal `pingpong` :

```

system :pingpong do
  inner :clk, :start

  [2].shared :pingpong
  arbiter(:arb).(pingpong)


  sequencer(clk,start) do
    sloop do
      arb <= 1
      pingpong <= 1
      step
      arb <= 0
    end
  end

  sequencer(clk,start) do
    sloop do
      arb <= 1
      pingpong <= 2
      step
      arb <= 0
    end
  end

  timed do
    clk <= 0
    start <= 1
    !10.ns
    clk <= 1
    !10.ns
    clk <= 0
    start <= 0
    !10.ns
    repeat(20) { clk <= ~clk ; !10.ns }
  end
end

```

Now, you should be used to it, so please try to simulate the code above. If you look at the VCD file in detail you will see a lot of signals but not any signal called `pingpong`. This is because shared signals hide underlining hardware that is exposed at simulation. Usually, what is relevant is the output value of the shared signal, which is called `<shared signal name>_out$<number>`. For our `pingpong` it is `pingpong_out$2`. Hence, you should get the following graph:

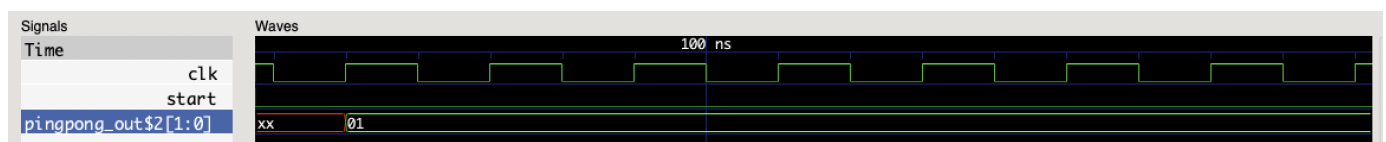

Well, this is not an interesting result: `pingpong` is always 1, what about the second sequencer? There are two reasons for this:

- By default, an arbiter gives priority to sequencers in order of declaration.

- When a sequencer is denied access, its write access is ignored and that's all.

Here, the first sequencer has higher priority and it happens that both always write to `pingpong` at the exact *same* time. For instance, if the second sequencer were delayed a bit compared to the first one, it would obtain access too:

```

system :pingpong do
  inner :clk, :start

  [2].shared :pingpong
  arbiter(:arb).(pingpong)


  sequencer(clk,start) do
    sloop do
      pingpong <= 1
      arb <= 1
      step
      arb <= 0
    end
  end

  sequencer(clk,start) do
    step
    sloop do
      pingpong <= 2
      arb <= 1
      step
      arb <= 0
    end
  end

  timed do
    clk <= 0
    start <= 1
    !10.ns
    clk <= 1
    !10.ns
    clk <= 0
    start <= 0
    !10.ns
    repeat(20) { clk <= ~clk ; !10.ns }
  end
end

```

And the simulation result should be:

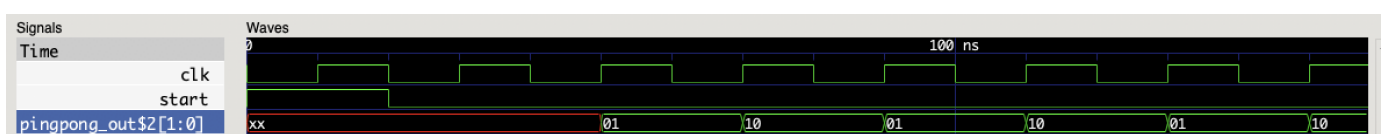

Still, it may be annoying that some writes of a sequencer can be ignored. In such a case, you can use a blocking version of the arbiter called the `monitor`. This module is used like the arbiter, but when write access is required, the sequencer will be blocked until the access is granted. Hence to avoid confusion, requiring access with a monitor is done by the `lock` method, and releasing it is done by the `unlock` one. For example, with the following code that only replaces `arbiter` with `monitor` in the initial one the expected pingpong exchange will happen:

```

system :pingpong do
  inner :clk, :start

  [2].shared :pingpong
  monitor(:arb).(pingpong)


  sequencer(clk,start) do
    sloop do
      pingpong <= 1
      arb.lock
      arb.unlock
    end
  end

  sequencer(clk,start) do
    sloop do
      pingpong <= 2
      arb.lock
      arb.unlock
    end
  end

  timed do
    clk <= 0
    start <= 1
    !10.ns
    clk <= 1
    !10.ns
    clk <= 0
    start <= 0
    !10.ns
    repeat(20) { clk <= ~clk ; !10.ns }
  end
end

```

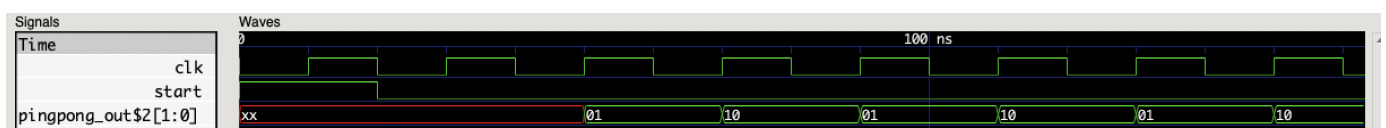As seen in the example, since the monitors locks processes, no `step` is required, and the simulation result should be:



WARNING: while with arbiter it was of no importance, with monitor the lock must be made *after* the shared signal is written, otherwise this value will be taken into account one cycle later.

By the way, why is there the `arbiter` module if the `monitor` does a better job? For performance reasons first: using an `arbiter` produces a small and faster circuit. It can be seen in the previous result: a monitor always waits for a cycle before granting access to one sequencer while the arbiter does it immediately. also, it is sometimes better not to block a sequencer: for example, maybe you want to write to a shared signal if possible, and if not do something else. this can be done as follows:

```
sequencer(clk,start) do
  arb <= 1
  if(sh.select == arb.cur_priority) { sh <= 2 }
  selse { <do something else> }
  arb <= 0
end
```

In the code above, the sequencer checks if it has access by comparing the shared signal selection with its priority (obtained by `arb.cur_priority`).

I do not like the priority rule of the arbiter/monitor

Indeed, sometimes we need to define our priority rules. This can be done when instantiating an arbiter or a monitor in two possible fashions:

- You can provide your priority table as an array containing the declaration order of the sequencers in order of priority, e.g., for reversing the priority in our example:

```
arbiter(:arb,[1,0]).(pingpong)
```

- You can provide your policy as a chunk of HDLRuby code whose argument is in the declaration order of a sequencer and that returns true if the sequencer is granted priority, e.g, for switching priority at each acquirement:

```
inner switch: 1
arbiter(:arb) { |i| switch <= ~switch ; i == switch }. (pingpong)
```

Now you know:

- That sequencers run in parallel.
- How to synchronize them.
- How to share resources between them.
- How to make intricate deadlocks and how to escape them using arbiters and monitors... Just to make even more intricate ones (trust me with that).
- And...

That's all for this section!

Congratulations! You know everything about describing a working circuit and using your knowledge of software design, I am sure you can already do great things.

But in hardware, you can go much more into the details for even more performance. So let us go to the more advanced parts of this tutorial.

4. How to add parallelism to your algorithms

In software, when you want to do parallelism you usually need specific libraries because the underlying model of software is inherently sequential. But this is not the case with sequencer because:

- [A sequencer is not a program](#)
- [Adding parallelism is genuine](#)

4.1. A sequencer is not a program

We said earlier that hardware is inherently parallel and we showed that multiple sequencers run concurrently by default. However, you may want to increase parallelism within an algorithm too: after all, it is what recent processors do, so why not hardware?

To tell the truth, we lied a little when we said that the sequencers were "executing" statements in order. They do not execute anything and statements are not *instructions*, rather, they are *instantiations* of circuits performing basic computations, and the sequencer only schedules when each circuit is to be used. For example, the following code describes two 3-value addition circuits selected respectively at the first and second clock cycles:

```
sequencer(clk,start) do
  d <= a + b + c
  step
  z <= u + v + w
end
```

And what about the followings:

```
sequencer(clk,start) do
  d <= a + b + c
  z <= u + v + w
end
```

... Yes, as said early, when there is no control statement or step, the clock does not advance. That means that both adder circuits are selected at the same time and do "run" in parallel. Then what about the following:

```
sequencer(clk,start) do
  d <= a + b + c
  z <= u + v + d
```

... This time, `z` requires the value of `d`, but both circuits will again be selected at the same time. However, the output of the first one is connected to the third input of the second one: since they are combinatorial, waiting a little bit is enough for obtaining the right `d` input for computing `z`.

WARNING: in hardware design with HDLRuby (actually common with all similar languages like Verilog VHDL or VHDL) is assumed that a clock is slow enough for the relevant combinatorial circuits to complete computation before the next cycle. If this is not the case, the resulting circuits will not function properly. Fortunately, the synthesis frameworks usually provide tools for verifying these timings.

4.2. Parallel control statements and enumerators

Sequencers provide many constructs for easy control and enumeration. However, those constructs are sequential by construction. What if you would like to do the same in parallel? This is possible, but there is an important restriction:

WARNING: there cannot be any loop within a parallel section of an algorithm.

4.2.1. Parallel conditionals

With that being said, even without loops you can do a lot of things. First, let us see parallel conditional and case statements. We already presented the sequential versions: `sif` and `scase`. The parallel versions have the same syntax but use an `h` instead of an `s`:

- `hif(<condition>) <block>` : executes `block` if `condition` is true (i.e., different from 0).
- `helsif(<condition>) <block>` : executes `block` if the previous `hif` or `helsif` condition is not met and if the current `condition` is met.
- `helse <block>` : executes `block` if the condition of the previous `sif` is false (i.e., equals 0). It is also used for giving the default block for the `hcase` statement (see below).
- `hcase(<choice>)` : initialize a multiple case statement.

WARNING: these are parallel statements, hence their blocks **CANNOT** contain any sequential statement like `step`, `sif`, `sloop`, or even `sbreak`.

However, they have the advantage of not waiting for the next clock cycle, hence high-speed algorithms can be devised when using them. For example, the following assigns to `d` the max of signals `u`, `v`, and `w` in less than one cycle:

```
sequencer(clk,start) do
  hif(u > v) do
    hif(u > w) { d <= u }
  else      { d <= w }
end
helsif(v > w) { d <= v }
helse      { d <= w }
...
end
```

4.2.2. Yes, but without loops, we are quite limited no?

There is a whole range of computations that do not require any loop: the **dataflow** computations. Indeed, more often than not, in software programs, the `for` loops and others are only there for ease of design or conciseness of code, and *do not* have any algorithmic purpose. For example, if you want to pick up the max value of a fixed-sized array, you do not need a loop for that... Heh, we just did that in the previous section (just replace `u`, `v`, and `w` with `ar[0]`, `ar[1]`, and `ar[2]`).

Still, the code of the previous section was only for three variables, and the code was already a bit messy. Indeed, it would be better to have clear code. Fortunately, you can use Ruby for this purpose... Do you remember? In HDLRuby, Ruby code is executed at compile time, so Ruby loops or iterators can be used to produce complex hardware descriptions cleanly. However...

WARNING: Ruby code itself does not generate nor interact with hardware, for obtaining real hardware description you **must** put HDLRuby code within the Ruby loops.

Also:

WARNING: Ruby iterators **do not** apply on HDLRuby construct. But, you can convert an HDLRuby signal to a Ruby array for applying Ruby iterators on it. For that purpose, please use the `to_a` method.

Let us wrap everything we said with a sequencer selecting in parallel the largest element of an array signal of 16 8-bit elements:

```
system :maxxer do
  inner :clk, :start

  bit[8][-8].inner ar: [ _h05, _hA3, _h54, _h2F, _h33, _hE4, _h6B, _h1C ]
  bit[8].inner :ar_max

  sequencer(clk,start) do
    ar_max <= 0
    ar.to_a.each do |e|
      hif(ar_max < e) { ar_max <= e }
    end
  end

  timed do
    clk <= 0
    start <= 1
    !10.ns
    clk <= 1
    !10.ns
    clk <= 0
    start <= 0
    !10.ns
    repeat(20) { clk <= ~clk ; !10.ns }
  end
end
```

The simulation result should be:



As promised, the max is obtained at the first cycle of the sequencer execution!

However, the following code will not produce anything other than setting `ar_max` to 0, because the Ruby `max` method does not use any HDLRuby code:

```
sequencer(clk,start) do
  ar_max <= 0
  ar.to_a.max
end
```

So, you can use `each` but not `max`. More generally:

If the method iterates without any **implicit** computation, then it can be used for parallel HDLRuby description.

Yes, this is becoming confusing because it is hard to know what Ruby does when executing its methods. Unfortunately, for now, there is nothing to help more, but we hope to clarify things in future versions of HDLRuby. For now, if unsure, it is recommended to stick to the following Ruby methods:

- `each` , `each_cons` , `each_slice`
- `reduce` (or `inject`)
- `zip`

Now you know:

- How to use Ruby code for concisely describing parallel HDLRuby code.

That's all for this section!

That was short this time because almost all have been already said in the previous sessions. But now it is time to go past the sequencers and dive into real RTL design.

5. Toward lower level hardware design: the processes

Why sequencers are easy to use with a software mindset, they are implemented on top of a control circuit that schedules their operations. While this circuit does not represent much overhead, you may want top-notch optimizations, or simply you may want more precise control over what hardware will be produced. It is therefore time to leave the comfort of the sequencer and study genuine hardware description constructs: the *processes*. Things will become messy, but here is an attempt to do it progressively:

- [What are the processes?](#)
- [What are the connection processes?](#)
- [What are the combinatorial processes?](#)
- [What are the clocked processes?](#)
- [What about the control statements in processes?](#)
- [How to share signals in processes?](#)

5.1. What are the processes?

First, we must make things clear:

Process in hardware has very little (nothing?) to do with any kind of software process.

In hardware, a process is a list of data flow statements that are activated (we would say **executed** if they were software instructions) on a common condition. Depending on the activation condition, there are three kinds of processes:

- The connection processes (in HDLRuby they are considered to be processes)
- The combinatorial processes
- The clocked processes

We will detail them in further sections, but there is another property of processes to discuss before: that is the way the data flow statements are scheduled within a process. Like with the sequencer between clock cycles, everything is parallel, but unlike it, there are two possible ways for handling dependencies:

- Blocking assignments scheduling where like with a sequencer, the result of a statement can be used directly as input of the following statements. Such processes are declared with the `seq` keyword.
- Non-blocking assignments where all the statements are independent of each other. Such processes are declared with the `par` keyword.

For example, if we assume that the initial value of `x` is 1 and that the initial value of `y` is 0, when the following process is activated, the value of `z` will become 4:

```
seq(<activation condition>) do
  y <= x + 1
  z <= y + 2
end
```

Whereas, with the following process, `z` will become 2, i.e., it will be the result of the addition of the initial value of `y` which is 0 to 2 :

```
par(<activation condition>) do
  y <= x + 1
  z <= y + 2
end
```

There is a couple of caveats with the non-blocking process. First, a signal is assigned twice, and only the last assignment prevails. For example, with the following process, assuming the same initial values for `x` and `y` as before, `z` will become 3 and not 2:

```
par(<activation condition>) do
  y <= x + 1
  z <= y + 2
  z <= y + 3
end
```

Second, the order of statements assigning to different values does not affect the result. For example, the following process is identical to the previous one:

```
par(<activation condition>) do
  z <= y + 2
  z <= y + 3
  y <= x + 1
end
```

But this one is different (we switched two assignments to the same signal):

```

par(<activation condition>) do
  y <= x + 1
  z <= y + 3
  z <= y + 2
end

```

Now let us see the different kinds of processes in detail.

5.2. What are the connection processes?

We already mentioned the connections at the beginning of this tutorial about how to [reuse circuits](#). Each connection is considered to be a standalone connection process. Such a process is continuously activated, and its left value is *always* equal to its right value.

Since the connection processes are one-statements only, they do not require a `seq` or `par` keyword. For example, the following module includes two connections to its output ports:

```

system :a_system_with_cnx do
  [8].input :x, :y
  [8].output :u, :v

  u <= x + y
  v <= x - y
end

```

5.3. What are the combinatorial processes?

These processes are declared with a `seq` or `par` keywords with a list of signals as activation conditions. They have activated each time one or more signals of their activation condition changed value. For example, the following process will only be activated when `x` or `y` changes value, but not when `z`, `u` or `v` does:

```

par(x,y) do
  u <= x + z
  v <= y - z
end

```

There is another kind of combinatorial process that is activated each time a signal depends on changes in value. They are declared with the `seq` or `par` keywords without any activation condition. For example, the following process will be activated when `x`, `y`, or `z` change value:

```

par do
  u <= x + z
  v <= y - z
end

```

Here is a more practical example: a circuit that computes the 8-bit checksum of an input 32-bit vector.

```

system :checksum do
  [32].input :x
  [32+8].output :z

  [8].inner :sum

  seq do
    sum <= x[31..24] ^ x[23..16] ^ x[15..8] ^ x[7..0]
    z <= [x,sum]
  end
end

```

In this code, the statement `z <= [x,sum]` concatenates the value of `x` with the value of `sum` using the concatenation operator `[]`.

Please note that the concatenation operator is different from the access operator even if they use the same characters: the syntax `<sig>[<integer or range>]` is the access operator, and the syntax `[<list of signals or values>]` is the concatenation operator.

You can check this module with the following simulation environment:

```


system :checksum_sim do
  [32].inner :x
  [40].inner :z

  checksum(:checksumI).(x,z)

  timed do
    x <= 0
    !10.ns
    x <= _h34F4AC68
    !10.ns
  end
end

```

The simulation result should be:

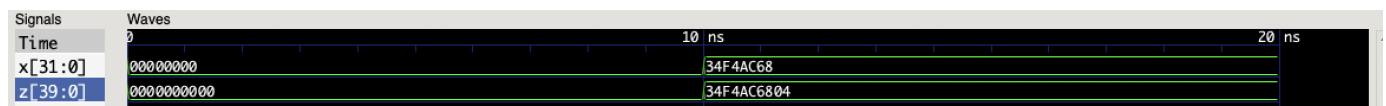

That is to say that the checksum of `x` is `04` appended at the end of `z`.

Combinatorial processes that are not a combinatorial circuit.

In the final hardware, a circuit whose output signals are also used as inputs are **not** a combinatorial circuit, and may not be a viable circuit at all. Such non-combinatorial circuits are used for making memory points (e.g., registers), or local synchronization (e.g., C elements). It is possible to describe such an element with a combinatorial process: it is enough to make a signal being dependent on itself in process. For example, for both combinatorial processes, signals `x` and `u` depend on themselves, and are therefore not describing combinatorial circuit:

```
par do
  x <= x + 1
end

seq do
  u <= v + 1
  v <= u + w
end
```

WARNING: while such processes are accepted in HDLRuby (as well as in other hardware description languages like Verilog HDL), it is strongly recommended **not** to use them because the behavior of the resulting circuit is hard to predict. If you want to use memory elements, you should use the clocked processes instead that will produce reliable circuits.

5.4. What are the clocked processes?

These processes are declared with the `par` or `seq` keyword with a list of signal edges as an activation condition. There are two kinds of signal edges:

- The positive edges indicate changes in single-bit signals from 0 to 1. They are noted as follows: `sig.posedge` where `sig` is a single-bit signal.
- The negative edges indicate changes in single-bit signals from 1 to 0. They are noted as follows: `sig.negedge` where `sig` is a single-bit signal.

These processes are usually used for describing parts of circuits that are synchronized by a global clock. This includes the cases where you want to memorize a value.

Here is a simple example for illustrating this kind of process:

```

system :clock_counter do
  input :clk, :run
  [32].output :count

  par(clk.posedge) do
    hif(run) { count <= count + 1 }
    helse    { count <= 0 }
  end
end


system :clock_counter_sim do
  inner :clk, :run
  [32].inner :count

  clock_counter(:clock_counterI).(clk,run,count)

  timed do
    clk <= 0
    run <= 0
    !10.ns
    clk <= 1
    !10.ns
    run <= 1
    repeat(30) { clk <= ~clk ; !10.ns }
  end
end

```

The result should be:

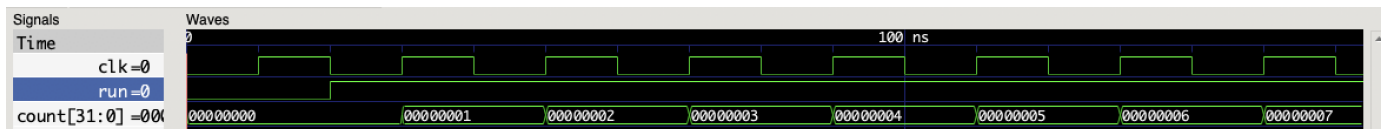

Did you get what the `clock_counter` circuit does? Yes, it simply counts the number of the positive edge of the signal `clk` when `run` is 1: signal `count` is initialized at 0 when declared, then the process which is activated on each positive edge of `clk` increases this signal by one. If you remember the sequencer, such kinds of processes look alike. Indeed, sequencers are built upon such processes. However, within processes, the fancy control statements like `sif`, `sloop`, or the enumerators **cannot** be used.

As seen in this code, a previously seen control statement has been used: the `hif`. If you remember well, that was for parallel computation in sequencers. But more generally, what can be used?

5.5. What about the control statements in processes?

There is not much to say in this section... Because all have been said in the section about [parallelism in sequencer](#). The fact is all the constructs described in this previous section are designed for the processes, and by extension can be used in sequencers.

These statements can be used for both clocked processes and combinatorial processes. For example, the following is a combinatorial circuit that implements a simple ALU (Arithmetic and Logic Unit), able to perform the addition, the subtraction, the bitwise AND, and the bitwise OR of the two input values, the operation is selected by a third input signal.

```

system :alu do
  [8].input :x, :y
  [2].input :opr
  [8].output :z

  par do
    hcase(opr)
    hwhen(0) { z <= x + y }
    hwhen(1) { z <= x - y }
    hwhen(2) { z <= x & y }
    hwhen(3) { z <= x | y }
  end
end

```

This circuit is combinatorial, hence every time `x`, `y`, or `opr` change value, `z` will also instantaneously change (in reality, there is a small physical delay that is not simulated).

You can check it as follows:

```


system :alu_sim do
  [8].inner :x, :y
  [2].inner :opr
  [8].inner :z

  alu(:aluI).(x,y,opr,z)

  timed do
    x <= _h2A
    y <= _h31
    opr <= 0
    !10.ns
    opr <= 1
    !10.ns
    opr <= 2
    !10.ns
    opr <= 3
    !10.ns
  end
end

```

The result should be:

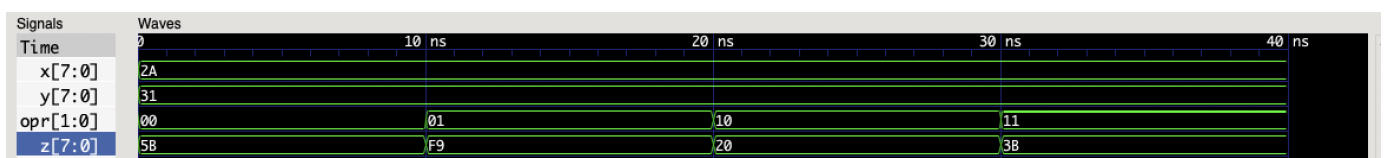

...So we can do controls with processes, but what about sharing signals?

5.6. How to share signals in processes?

This is the last feature of the sequencer: signals that can be written to by multiple sequencers. But can we do the same with processes?

- The short answer is no: the shared signals and the arbiter or monitor constructs can only be used in sequencers.
- The long answer is yes, there are even two possible ways, but you will have to describe the underlying hardware from scratch.

5.6.1. The first way: use a multiplexer.

A multiplexer is a circuit that selects one input among several ones to be output. Usually, this is done according to an additional input that indicates the number of the selected input. In HDLRuby, there are two simple ways to describe multiplexers:

- The use of the `hcase` statements. We had an example previously with the ALU:

```
system :alu do
  [8].input :x,:y
  [2].input :opr
  [8].output :z

  par do
    hcase(opr)
    hwhen(0) { z <= x + y }
    hwhen(1) { z <= x - y }
    hwhen(2) { z <= x & y }
    hwhen(3) { z <= x | y }
  end
end
```

With this example, all the operations are performed in parallel, and the `hcase` statement selects which result is to be sent to `z` according to the selection signal `opr`.

- The use of the `mux` operator that has the following syntax: `mux(<selection>,<input 0>,<input 1>, ...)` where `selection` is the selection signal, and the other arguments are the possible inputs. The same ALU circuit can therefore be described as follows:

```
system :alu do
  [8].input :x,:y
  [2].input :opr
  [8].output :z

  z <= mux(opr, x+y, x-y, x & y, x | y)
end
```

For this second example, a connection is used instead of a combinatorial process since there is a single statement.

5.6.2. The second way: use of tri-state bus

Multiplexers are easy to describe and use but their size grows exponentially with the number of inputs and linearly with their bit width. Moreover, the number of inputs of a chip is usually more strongly limited than their size. For all

these reasons, an alternative is sometimes used: the tri-state buses. They are signals where several processes or circuits can write a value provided that only one does it at a time and that when not writing the accesses are set in high impedance.

Before explaining further the tri-state buses, we need to clarify a possible misconception about hardware values: we often spoke about bits, and it was probably assumed that their possible values were 0 or 1 for standard boolean logic. However, in hardware design it is common to use a 4-valued logic that represents the relevant states of a wire in a circuit:

- 0 for ground level, used for representing `false` or the digit 0 ;
- 1 for power supply level, used for representing `true` or the digit 1 ;
- Z for high impedance, used in tri-state buses;
- X for undefined level, usually indicates a problem in the circuit or an uninitialized state.

Physically, when a signal is set to the Z state, it is possible to safely write another value on it, its state becoming this written value. Such a signal is then called a tri-state signal or bus.

Three state signals can be `inner` , `inout` , and `output` , and in theory, as long as there are no simultaneous 0 or 1 writes on them, they can be used freely. However, in practice, synthesis tools prioritize safety over flexibility and will reject several descriptions that should work. This is highly dependent on the tool you are using, hence we cannot give precise guidelines for the proper use of such signals. Instead, here is an example of tri-state bus usage that is guaranteed to work with a majority of the design tools, please feel free to adapt it to your needs:

```

system :ram8 do
  input :clk, :en, :rwb
  [8].input :addr
  [8].inout :data

  bit[8][-2**8].inner :content

  [8].inner :tmp

  par do
    hif(en & rwb) { data <= tmp }
    helse          { data <= _bZZZZZZZZ }
  end

  par(clk.posedge) do
    hif(en) do
      # Read case
      hif(rwb) { tmp <= content[addr] }
      helse   { content[addr] <= data }
    end
  end
end

```

```

system :ram8_sim do
  inner :clk, :en, :rwb
  [8].inner :addr, :data

  [8].inner :value

  ram8(:ram8I).(clk,en,rwb,addr,data)

  par do
    hif(en & ~rwb) { data <= value }
    helse          { data <= _bZZZZZZZZ }
  end
end

```

```

timed do
  addr <= 0
  en   <= 0
  rwb  <= 1
  value <= 0
  clk  <= 0
  !10.ns
  clk  <= 1
  !10.ns
  repeat(256) do
    en   <= 1
    rwb  <= 1
    clk  <= 0
    !10.ns
    clk  <= 1
    !10.ns
  end
end

```


```

en    <= 0
addr  <= addr + 1
value <= value + 1
clk   <= 0
!10.ns
clk   <= 1
!10.ns
en    <= 1
rwb   <= 0
clk   <= 0
!10.ns
clk   <= 1
!10.ns
en    <= 0
clk   <= 0
!10.ns
clk   <= 1
!10.ns

end
end
end

```

And the simulation result should be:

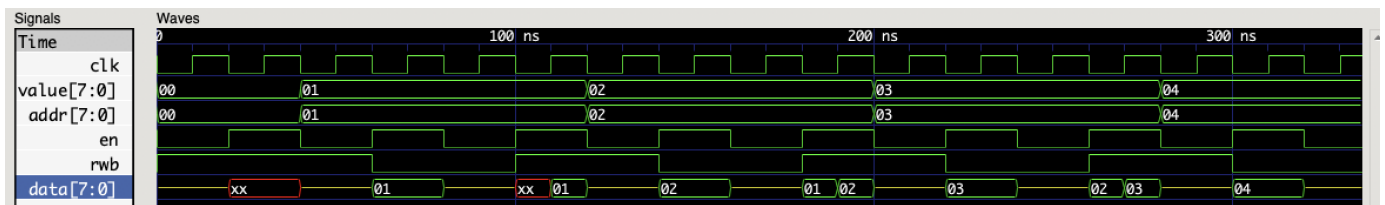

The first module is an 8-bit address 8-bit data RAM with a single data bus for both reading and writing. When the RAM is not read (en is 0 or rwb is 0), the data bus is set to Z . The second module simply accesses the RAM, and for that purpose uses a process specifically for writing to the data bus: when a write operation is performed (en is 1 for activating the access to the RAM and rwb is set to 0), the value is written to the bus, otherwise, a value is nonetheless written but it is a Z value. The coding style of this process is crucial for ensuring synthesis tools will succeed: we cannot guarantee it will work if it is described differently.

This section was quite a leap from the software mindset that represents processes...

But, now you may understand:

- How to describe low-level hardware with HDLRuby with processes.
- The existence of three kinds of processes: the connections, combinatorial, and clocked processes.
- How to use controls in processes.
- How to write several values to a single signal without the comfort brought by the sequencers and their shared signals.
- What is a tri-state bus and how to use it?

With that, you have all the constructs required for describing optimized hardware. Of course, mastering them requires a lot of know-how, but this is out of the scope of this tutorial. To go further, please follow lessons about hardware design using popular hardware description languages like Verilog HDL or VHDL since what you can do with them, you can do it with HDLRuby.

However, there remains a few major features for more efficient coding inherited from the Ruby language.

6. Not enough? What about genericity, object orientation, metaprogramming, and reflection?

Let us imagine you spent hours designing a circuit processing 8-bit values for outputting a 16-bit result and you learn that the input should be 16-bit and the output 8-bit. Well, that's not so tough, you just need to modify the data types in your circuit description... **everywhere**. When you just finished, you learn that it would be great if there was also another version of the circuit that could output flags about the result. Ok, so let us make another version of the circuit, since not much is different, let us do some copy and paste and made the modifications for the flags... But whoop! You did not notice that with your modifications you unintentionally modified a few lines of code introducing new bugs... And of course, you realize it after hours of testing.

Such situations happen all the time in software design... But it is much worse in hardware. Indeed, due to the variety of hardware circuits, it is very common to want to reuse a design with different bit widths. This is why, existing hardware description language support genericity to a certain degree. However, HDLRuby ruby goes farther in term of genericity, and also add object-oriented programming, metaprogramming and reflection concepts to maximize the possibilities of code reuse. From now on, let us detail:

- [Genericity in HDLRuby](#)
- [Object-oriented programming in HDLRuby](#)
- [Metaprogramming and reflection in HDLRuby](#)

6.1. Genericity in HDLRuby

In HDLRuby, genericity is supported through the *generic module* constructs. These constructs describe circuits like standard module does, but with the addition of parameters that control their content. They are declared as follows:

```
system :<name> do |<list of parameters>|
  <some hardware description code>
end
```

The list of parameters is simply a list of variable names that can represent anything, e.g., some values of any type, some data types, or even some chunks of Ruby or HDLRuby code.

Before being used, a generic module must be specialized by specifying each of its parameters. This is done as follows:

```
<generic system>(<list of objects>)
```

Where `generic system` is the name of the generic module to specialize.

And there is nothing more to explain since there is no restriction with the parameters. Instead, here are a couple of examples. First, a module counting the clock cycles whose counter bit width is a generic parameter:

```

system :counter do |size|
  input :clk, :rst
  [size].output :count

  par(clk.posedge) do
    hif(rst) { count <= 0 }
    helse    { count <= count + 1 }
  end
end

```

If you want to instantiate this circuit, you will need first to specialize it. For example, here are two instances, named `counterI8` and `counterI16` that have respectively a 8-bit and a 16-bit output:

```

counter(8).(:counterI8)
counter(16).(:counterI16)

```

The second example is again a counter of clock cycle but whose full data type of the output is a generic parameter (not only its size), and whose has a given value that when reached triggers some hardware code also provided as a generic parameter:

```

system :counter_ext do |typ, trig, code|
  input :clk, :rst
  typ.output :count

  seq(clk.posedge) do
    hif(rst) { count <= 0 }
    helse do
      count <= count + 1
      hif(count == trig) { code.call(count) }
    end
  end
end

```

There is more to unwrap here:

- `typ` is the data type of the output, and is therefore used as is for declaring `count`
- `trig` is the value that will activate the hardware provided as a generic parameter.
- `code` is a chunk of HDLRuby code. To paste this code chunk in HDLRuby, the `call` method is used. For giving access to the `count` signal to this code chunk, it is passed as an argument of the method.

And here is one instance of this module called `counter_extI`, with a 16-bit signed output, a trigger at value 5, and a trigger code that sets the count to -4:


```

system :counter_ext_sim do
  inner :clk, :rst
  signed[16].inner :count
  counter_ext(signed[16], 5, proc { |count| count <= -4 }).(:counter_extI).
  (clk, rst, count)

  timed do
    clk <= 0
    rst <= 0
    !10.ns
    clk <= 1
    !10.ns
    clk <= 0
    rst <= 1
    !10.ns
    clk <= 1
    !10.ns
    clk <= 0
    rst <= 0
    repeat(20) { !10.ns; clk <= ~clk }
    !10.ns
  end
end

```

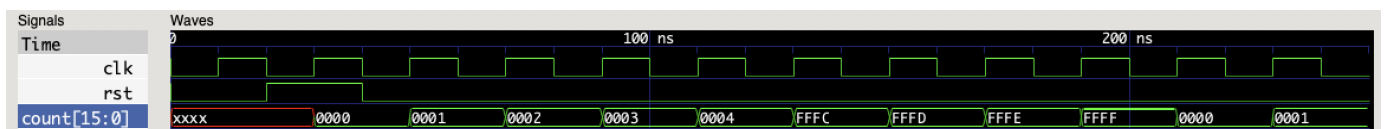In this code, the syntax `proc <block>` is for creating a chunk of HDLRuby (or Ruby) code from the content of `block`. With this environment, the simulation result should be:



6.2. Object-oriented programming in HDLRuby

Genericity allows using a single design for several different circuits but it does not allow modifying this design. This possibility is brought by object-oriented programming and its key concept: [inheritance](#). With it, it is possible to modify afterward a circuit design without touching the original description, to define a new circuit based on an original one without redoing everything from scratch, and to change a single instance of a circuit without influencing the other ones, all that with a simple [construct](#). Finally, it is possible under certain conditions to [reimplement parts of the code](#).

6.2.1 Inheritance

In HDLRuby, inheritance can be applied to modules. When a module inherits from another module, the latter is called its superclass module. By default, a module contains all the ports and all the content of its superclass modules. Then, new ports or content can be added to the later at will. Inheritance is declared as follows:

```

system :<name>, <list of superclass modules> <block>

```

Alternatively, the following syntax is also possible:

```

system :<name> do
  include <list of superclass modules>
  <HDLRuby code>
end

```

For example, let us consider the following 8-bit adder/subtractor module:

```

system :addsub8 do
  input :s
  signed[8].input :x, :y
  signed[8].output :z

  par do
    hif(s) { z <= x - y }
    helse { z <= x + y }
  end
end

```

And let us assume we want to design a new 8-bit adder/subtractor module that also outputs a zero flag. That can be done with inheritance as follows:

```

system :addsub_zf8, addsub8 do
  output :zf

  zf <= (z == 0)
end

```

So why is there an alternate syntax with the `include` keyword? This is for easing the mix of genericity and inheritance. For example, the previous circuit was 8-bit only. What if you want to do the same with generic input and output widths? For the initial counter, this is straightforward:

```

system :addsub do |width|
  inner :s
  [width].input :x, :y
  [width].output :z

  par do
    hif(s) { z <= x - y }
    helse { z <= x + y }
  end
end

```

But for the second one? It needs to transmit its generic parameter to its superclass module, but the parameter is only available within its block description. In such a case, the second syntax is useful:


```
system :addsub_zf do |width|
  include addsub(width)
  output :zf

  zf <= (z == 0)
end
```

6.2.2. Modifying a module or an instance

Let us assume that you think that after all, the adder-subtractor circuit you described previously should definitively have a `zf` flag for your new project. You can of course create a new module with inheritance for that, but you can also modify afterward the initial `addsub` module using the `open` method as follows:

```
addsub.open do
  output :zf

  zf <= (z == 0)
end
```

After that, all the instances that are created from `addsub` will include the `zf` flag computation and output.

In contrast, you may want that only one instance has the flag. In such a case, it may not be necessary to define a new module for that but just modify this instance only. This is possible using again the `open` method but on the instance. For example with instance used in the following simulation environment:

```

system :addsub_sim do
  signed[8].inner :x, :y, :z
  inner :zf, :s

  addsub(signed[8]).(:addsubI8).(s,x,y,z)

  addsubI8.open do
    output :zf


    zf <= (z == 0)
  end

  zf <= addsubI8.zf

  timed do
    x <= 0
    y <= 0
    s <= 0
    repeat(3) { !10.ns; x <= x + 1 }
    repeat(3) { !10.ns; y <= y + 1 }
    s <= 1
    repeat(3) { !10.ns; x <= x - 1 }
    repeat(3) { !10.ns; y <= y - 1 }
    !10.ns
  end
end

```

And the simulation result should be:

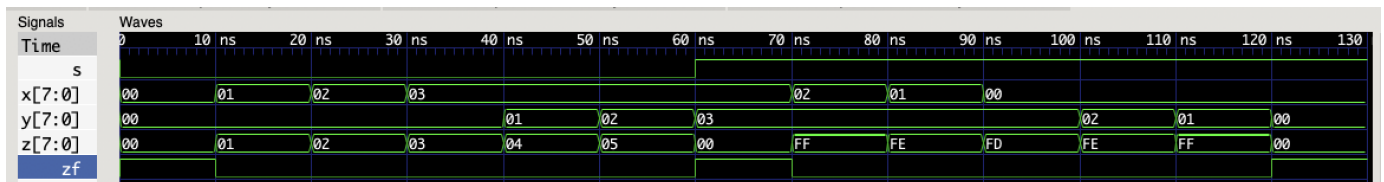

6.2.3. Overriding

Let us consider the following circuit that performs an addition and computes four flags:

```

system :adder_flags do |width|
  signed[width].input :x, :y
  signed[width].output :z
  output :cf, :zf, :sf, :of

  [cf,z] <= x.as(signed[width+1]) + y

  zf <= (z == 0)
  sf <= z[-1]
  of <= (~(x[-1]^y[-1])) - z[-1]
end

```

And let us assume we want to make a circuit that does the same but saturates the addition result between -300 and +300. For that purpose, the computation of `z` must be replaced. This is called `overriding` and for sake of code readability overriding is only permitted for the *named sub-section* of a module. A named subsection is declared as follows:

```
sub(<name>) <block>
```

Where `block` can contain any HDLRuby code apart from the port definition. A subsection can be overridden anywhere in the code, and also in subclass modules by redefining it. In our previous example, if `adder_flags` is rewritten as follows:

```
system :adder_flags do |width|
  signed[width].input :x, :y
  signed[width].output :z
  output :cf, :zf, :sf, :of

  sub(:add) do
    [cf,z] <= x.as(signed[width+1]) + y
  end

  zf <= (z == 0)
  sf <= z[-1]
  of <= (x[-1] & y[-1] & ~z[-1]) | (~x[-1] & ~y[-1] & z[-1])
end
```

Then a new module with saturated addition can be defined as follows using inheritance and overriding:

```
system :adder_sat_flags do |width|
  include adder_flags(width)

  sub(:add) do
    seq(x,y) do
      [cf,z] <= x.as(signed[width+1]) + y
      hif(z<-300) { z <= -300 }
      hif(z>300) { z <= 300 }
    end
  end
end
```

If you wish to see how this adder with saturation works, here is a simple simulation environment for it:

```


system :adder_sat_flags_sim do
  signed[16].inner :x, :y, :z
  inner :cf, :zf, :sf, :of

  adder_sat_flags(16).(:adderI).(x,y,z,cf,zf,sf,of)

  timed do
    x <= 0
    y <= 0
    repeat(3) { !10.ns; x <= x + 1 }
    repeat(3) { !10.ns; y <= y + 1 }
    !10.ns
    x <= 299
    y <= 0
    repeat(3) { !10.ns; x <= x + 1 }
    !10.ns
    x <= -1
    y <= -300
    repeat(3) { !10.ns; x <= x + 1 }
    !10.ns
  end
end

```

And the simulation result should be:

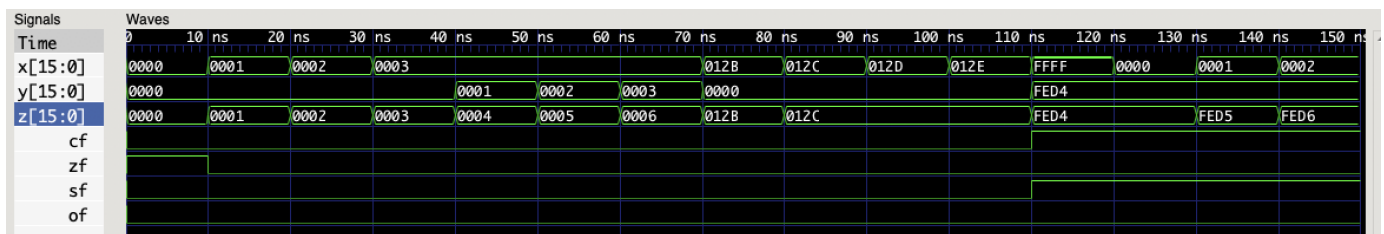

Note: with this circuit, the `of` flag (overflow) is always 0 because there cannot be any overflow for a 10-bit number with saturation at -300, 300.

6.3. Metaprogramming and reflection in HDLRuby

There is not much to say about metaprogramming and reflection because both have been used extensively in this tutorial.

- Metaprogramming consists in using programs that generate the final code. In HDLRuby, this is done by using Ruby code for generating, passing as an argument, and appending chunks of HDLRuby code. This has been done when presenting how to describe parallel code in sequencers, but this can be used everywhere, e.g., within the process too. Moreover, the possibility to use a chunk of code as a generic argument presented in this section is also metaprogramming.
- Reflection has been used in several cases, e.g., the `width` method for knowing the bit width of a type or the `open` method. For generally, HDLRuby provides a large number of methods for inspecting and modifying directly the objects of the internal representation. Please consult the documentation of the HDLRuby classes for details about them (good luck, this is low-level coding documentation).

Note: the sequencers, shared signals, arbiter, and monitor are not native HDLRuby constructs, they have all been implemented with metaprogramming and reflection.

